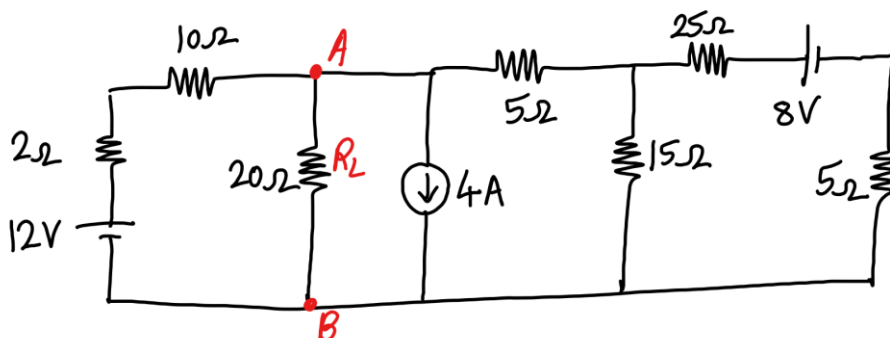
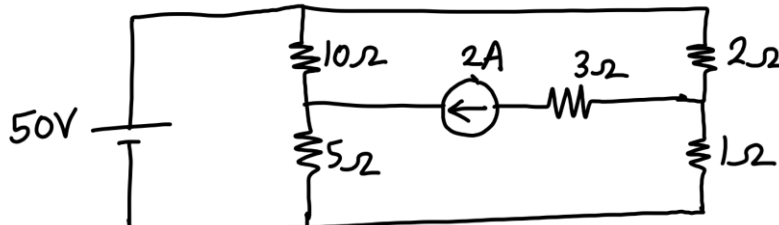
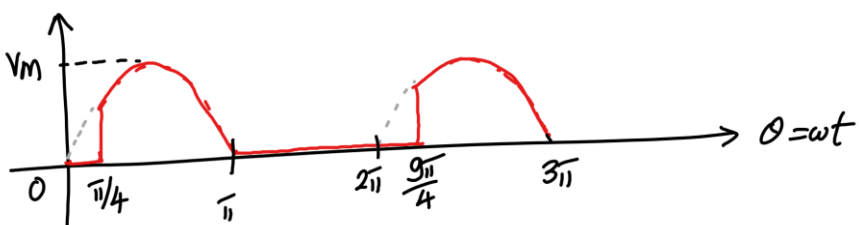
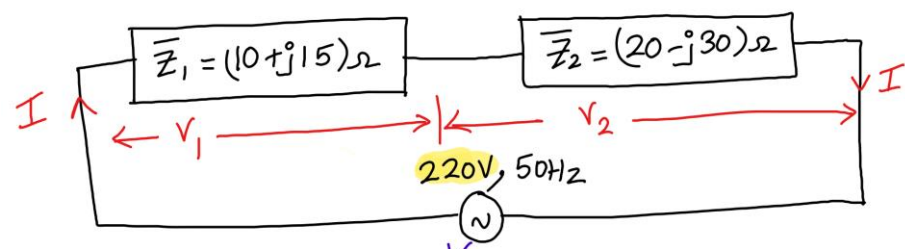




SOMAIYA
VIDYAVIHAR UNIVERSITY

Semester: July 2023 –Dec 2023		
Maximum Marks: 30	Examination: RE- In-Semester Examination	Duration: 1 Hr 15 Min
Programme code: 06 Programme: B.Tech	Class: FY	Semester: I (SVU R-2023)
Name of the Constituent College: K. J. Somaiya College of Engineering	Name of the department: COMP/ETRX/EXTC	
Course Code: 216U06C106	Name of the Course: Elements of Electrical and Electronics Engineering	

Question No.		Max. Marks
Q1	Obtain the power drawn by 20Ω resistor using Thevenin's theorem 	10M
Q2	Calculate the current flowing through 5Ω resistor using Mesh analysis 	10M
Q3	Find the average and the rms values of the waveform shown below: 	10M
OR		
Q3	For the circuit shown below, find current I , voltages V_1 & V_2 and power factor 	10M