



Amplitude Modulators

Circuits

Complied By:
Kartik R. Patel
EXTC Department
KJSSE, SVU

Basics of Modulators

Two approach of AM generation

- 1) Flywheel effect of Tank circuit (L and C) which has high Q factor.
- 2) Applying modulating signal and carrier signal to mixer (Non linear device).

Basics of Modulators

High Level Modulators:

Modulation takes place in the final element of final stage where carrier is at maximum amplitude.

Low Level Modulators: Modulation takes place prior to the output element of the final stage of transmitter.

I) Nonlinear mixing approach

- Non-Linear Analog device
- Frequency Translator


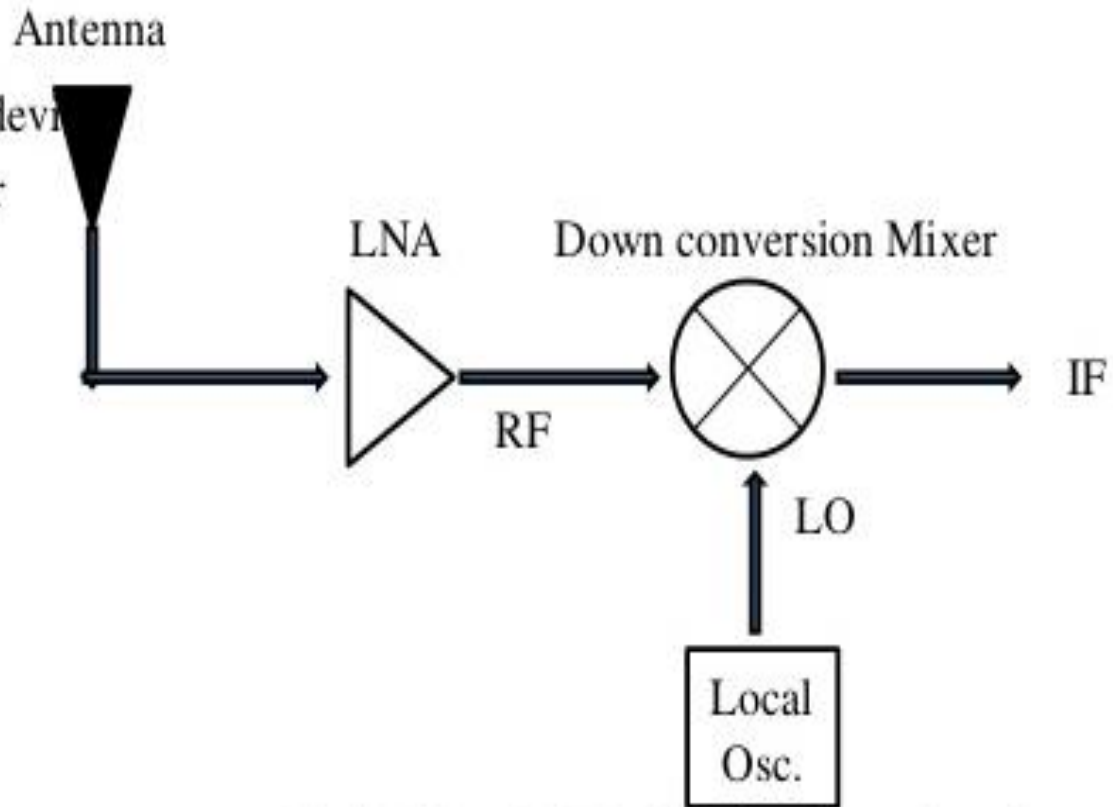


Fig.1: RF Front End / Role of mixer in generic receiver

If the inputs are sinusoids,
the ideal mixer output is the sum and difference frequencies given by

$$V_o = [A_1 \cos(\omega_1 t)] [A_2 \cos(\omega_2 t)] = \frac{A_1 A_2}{2} [\cos(\omega_1 - \omega_2)t + \cos(\omega_1 + \omega_2)t]$$

Low Level AM Modulator (Emitter)

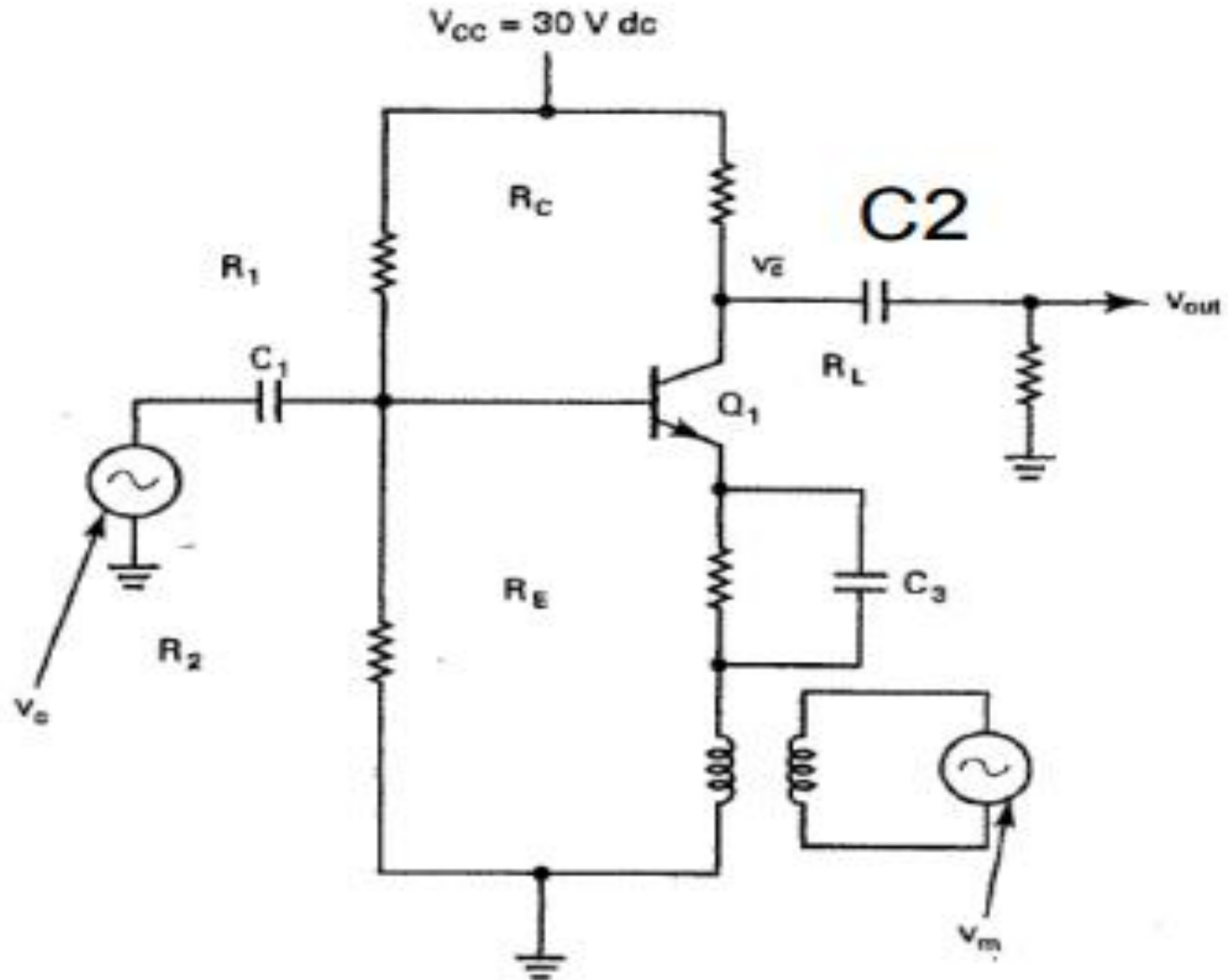

Low Level Modulators (Emitter)

- If $V_m(t) = 0 \rightarrow$ amplifier will be in **linear** mode
 - $\rightarrow A_{out} = V_c \cos(\omega_c t)$; V_c is voltage gain (unit less)
- If $V_m(t) > 0 \rightarrow$ amplifier will be in **nonlinear** mode
 - $\rightarrow A_{out} = [V_c + V_m \cos(\omega_c t)] \cos(\omega_c t)$
- $V_m(t)$ is isolated using T1
 - The value of $V_m(t)$ results in Q1 to go into cutoff or saturation modes
- C2 is used for coupling
 - Removes modulating frequency from AM waveform

Low Level Modulators

The Voltage gain is given by:

$$A_v = A_q [1 + m \sin(2\pi f_m t)]$$

where A_v = amplifier voltage gain with modulation (unitless)

A_q = amplifier quiescent (without modulation) voltage gain (unitless)

$\sin(2\pi f_m t)$ goes from a maximum value of $+1$ to a minimum value of -1 .



$$A_v = A_q(1 \pm m)$$

where m equals the modulation coefficient. At 100% modulation, $m = 1$,


$$A_{v(\max)} = 2A_q$$

$$A_{v(\min)} = 0$$

Low Level AM Waveforms

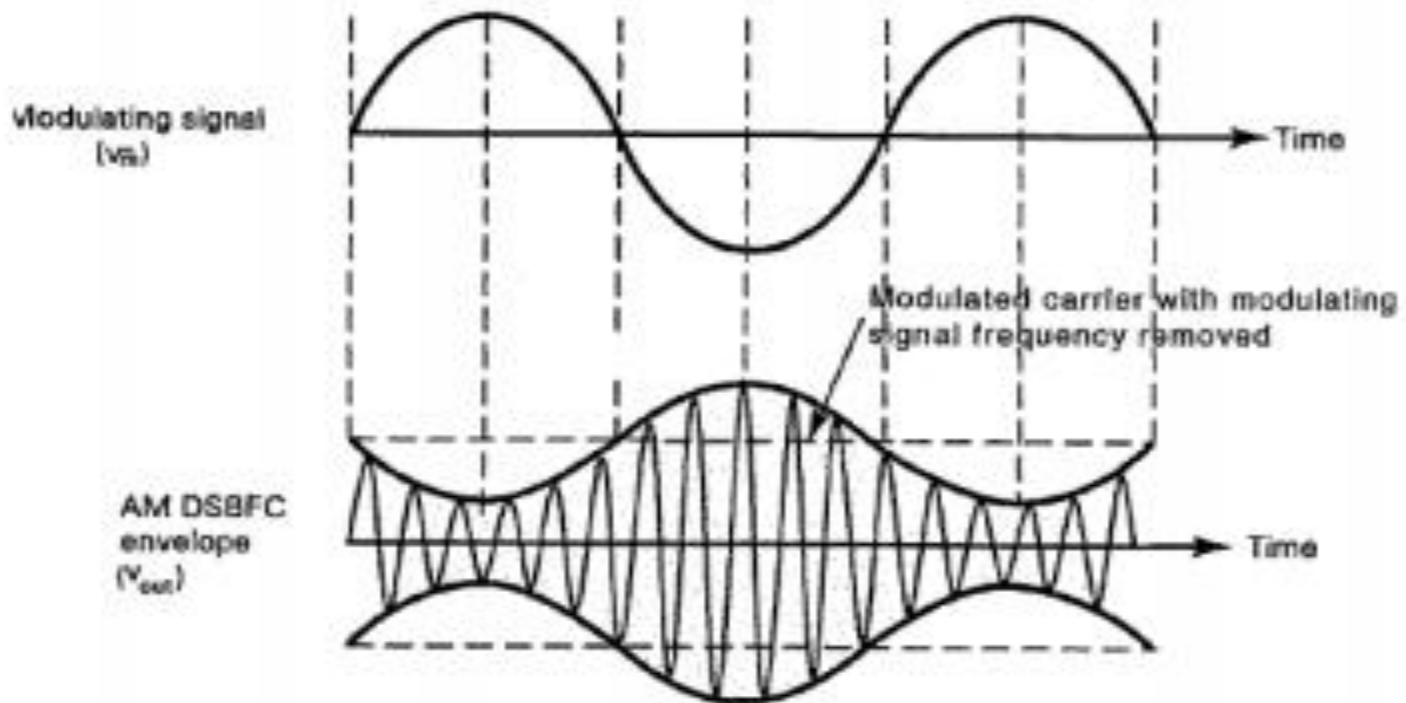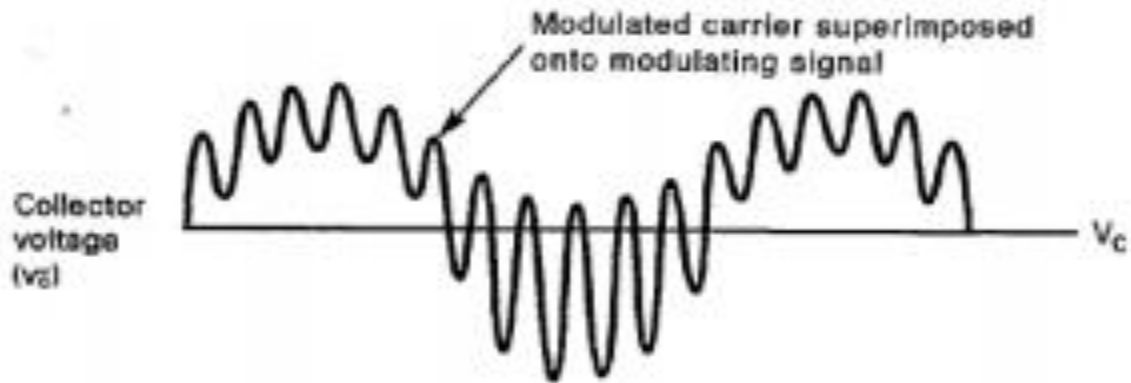


2) Flywheel effect of Tank circuit

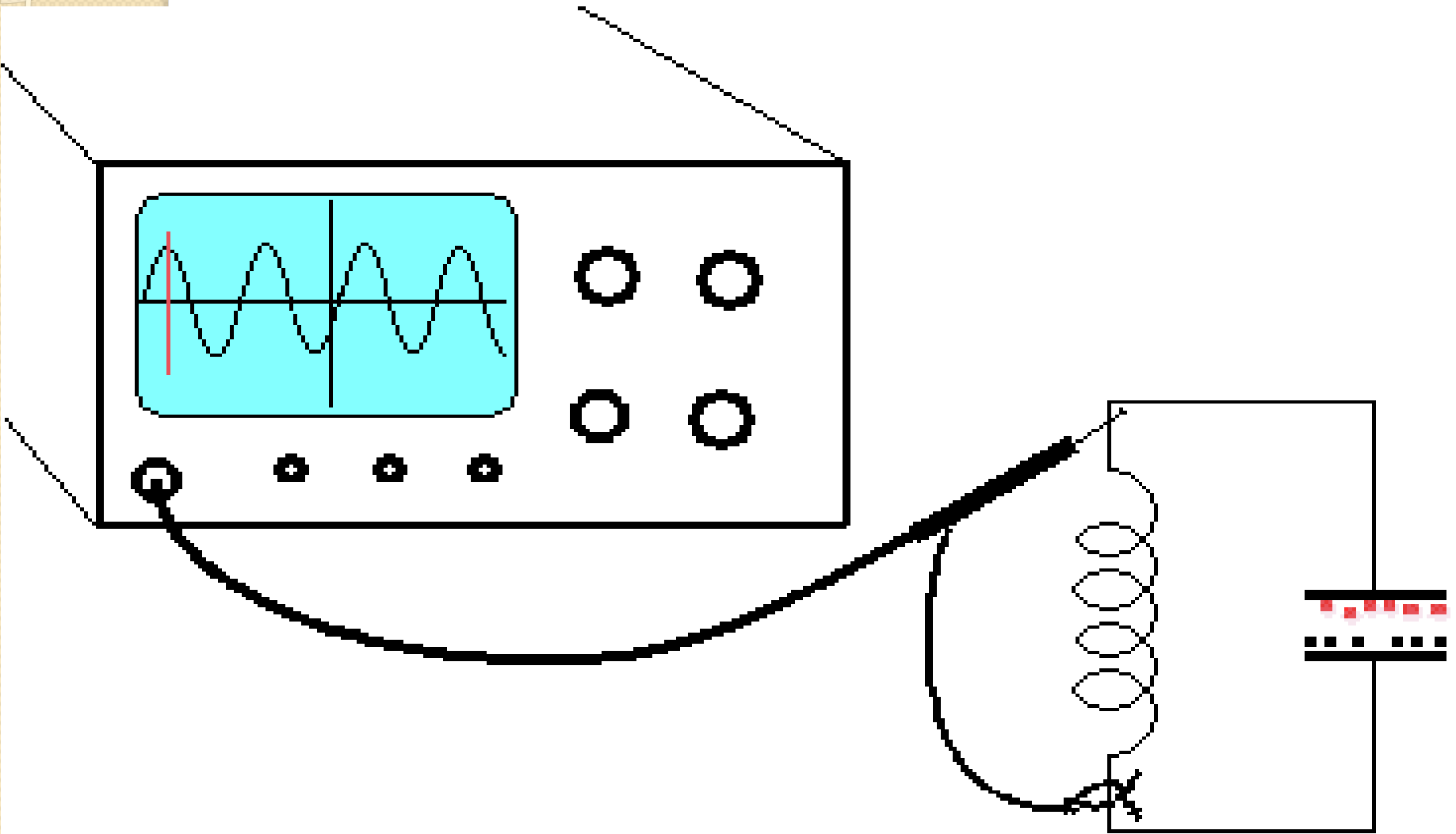


THE CRO MONITORING A TUNED CIRCUIT

Flywheel effect of Tank circuit

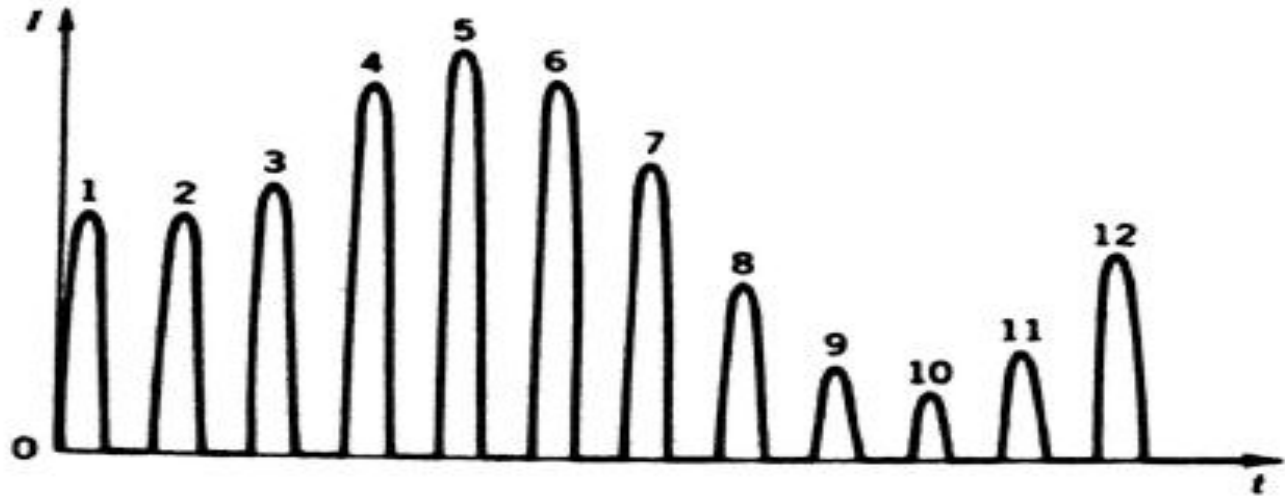


(a) Current pulses to tuned circuit

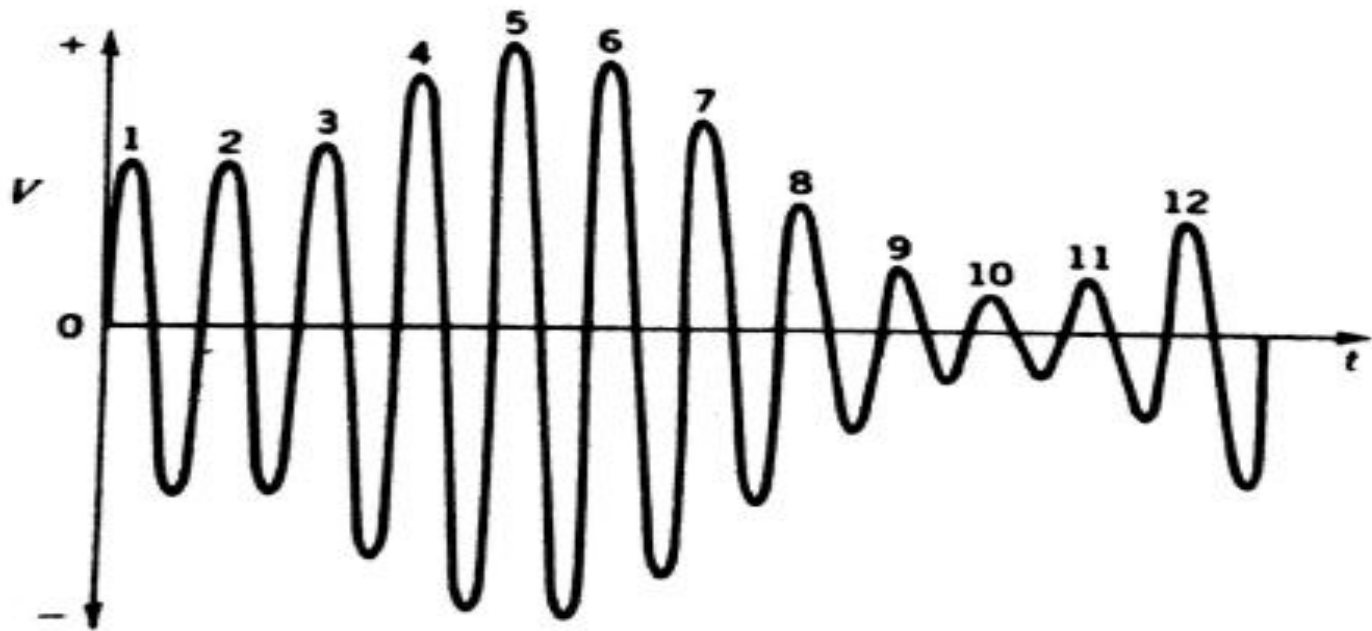


(b) Tuned-circuit AM voltage.

Medium Power AM Modulator

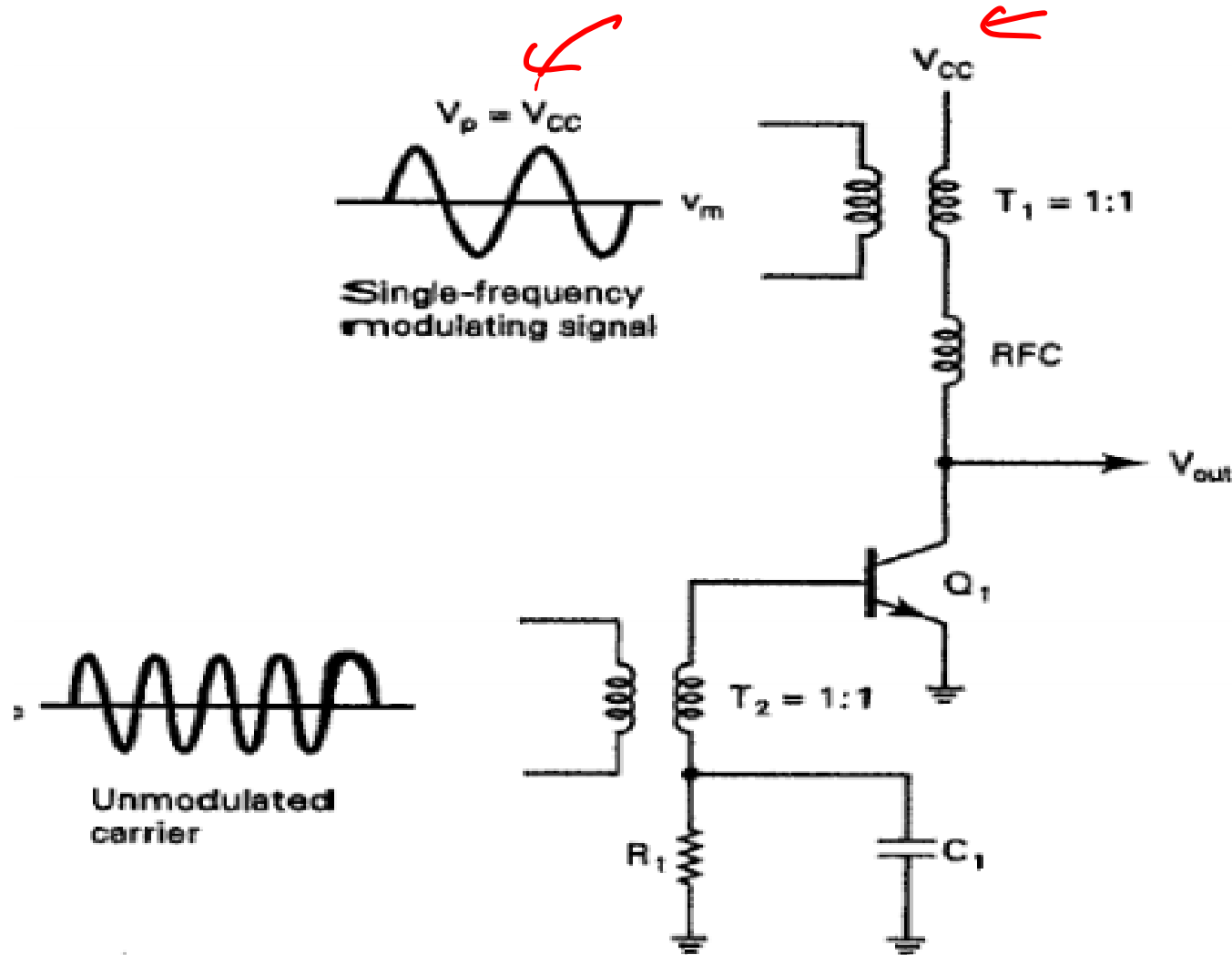

NO modulating signal

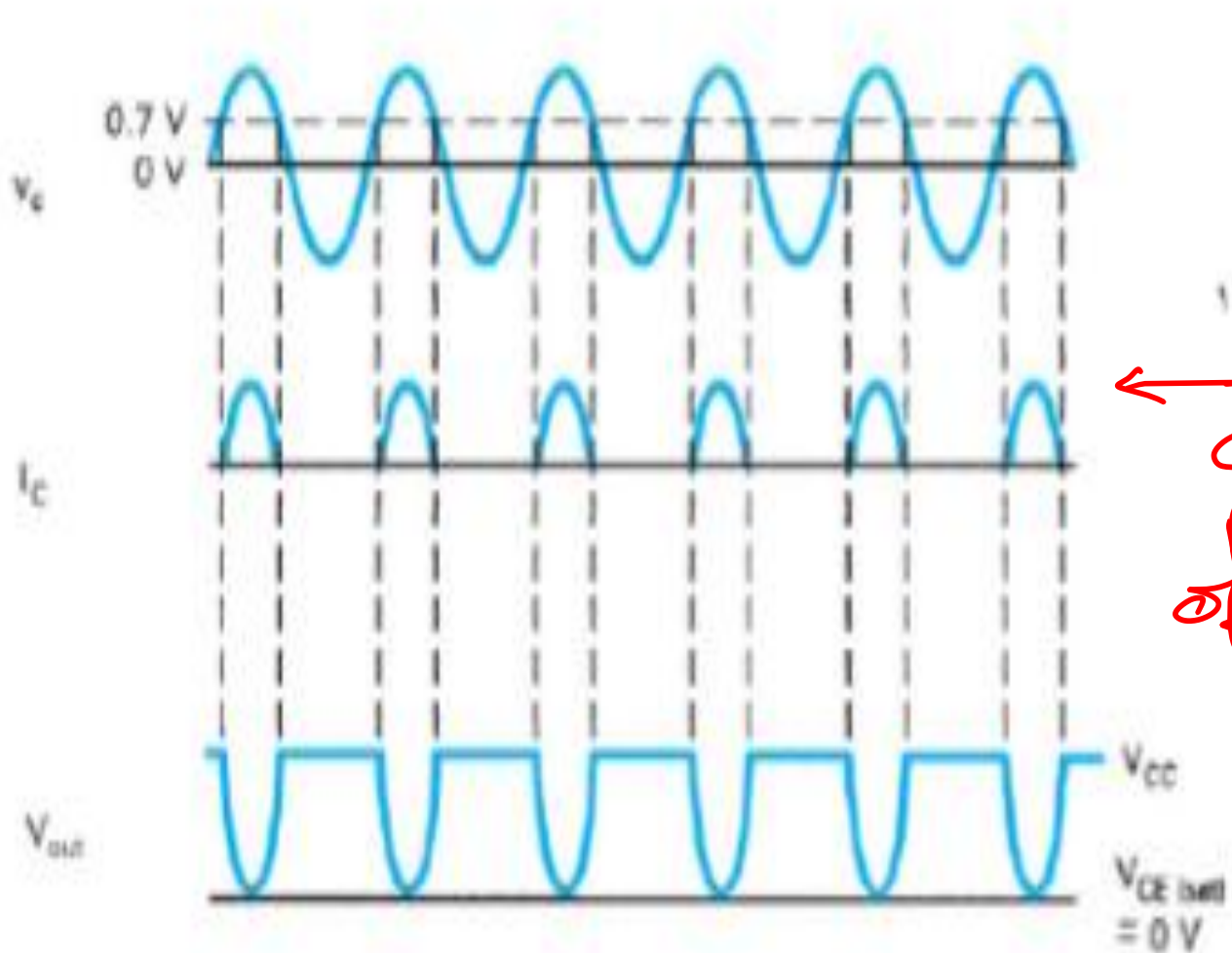


← All current pulses are of equal

With Modulating Signal

$$V_{om} = V_{cc}$$



Modulating Signal

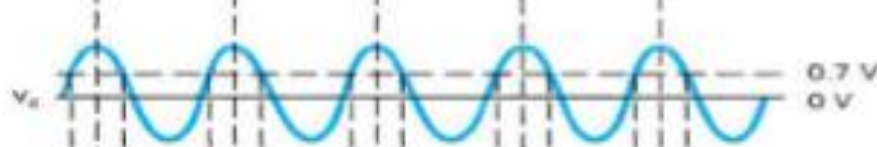


Voltage across collector



current pulse amplitude changes as per V_m
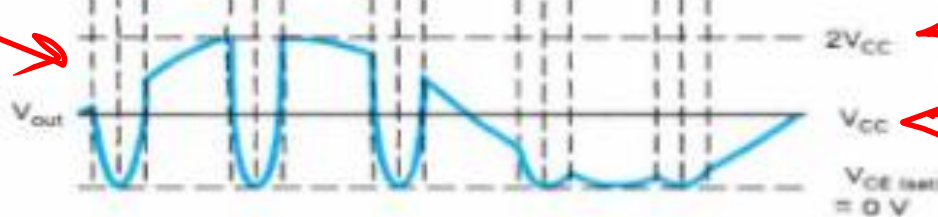
$$\begin{aligned} \text{Max} &= 2V_{cc} \\ \text{Min} &= 0V \end{aligned}$$




$2V_{cc}$

V_{cc}


$V_{ce(sat)} = 0V$

$0V$

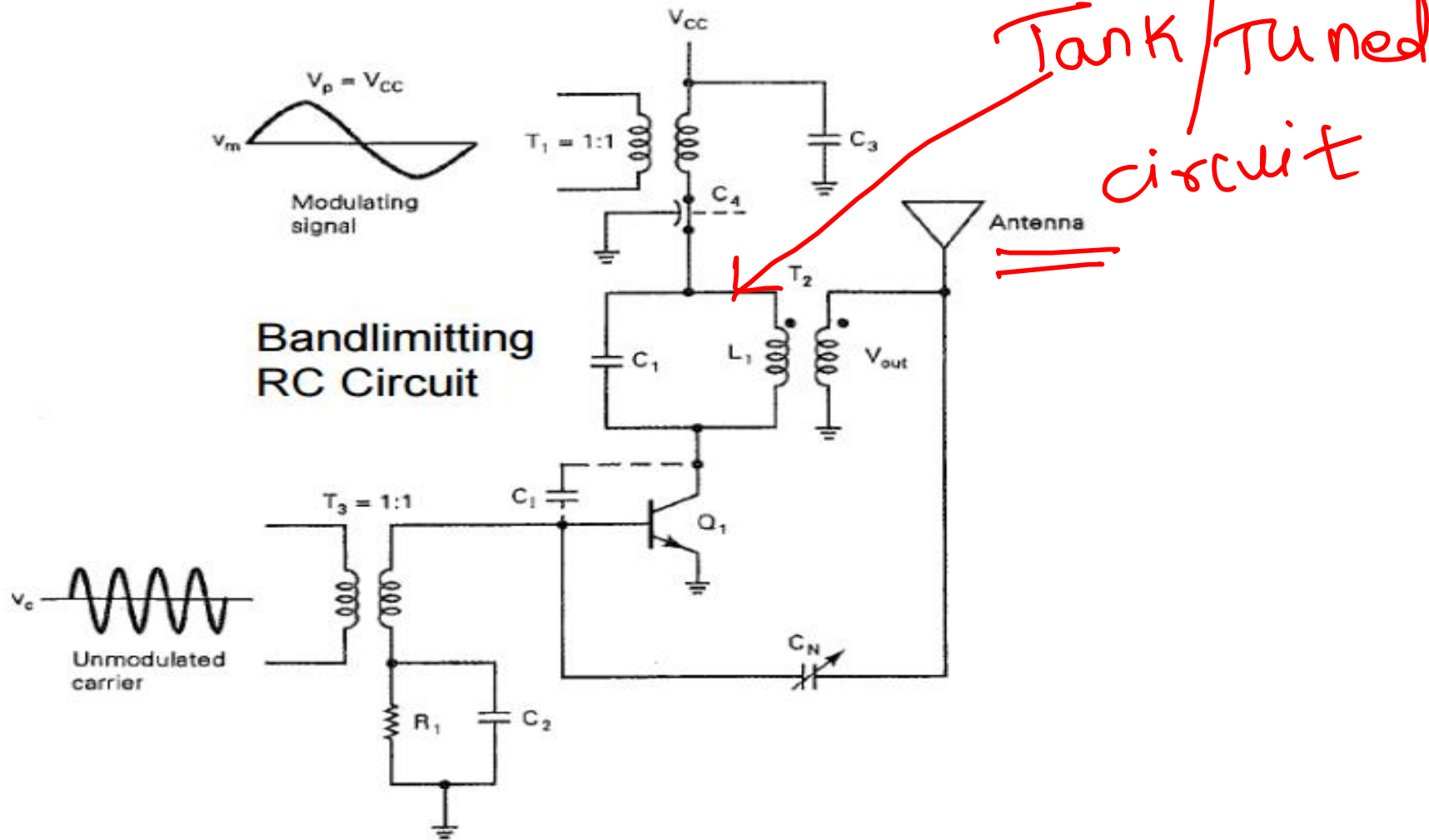Medium Power AM Modulator(More Practical circuit)



Medium Power AM Modulator Waveforms

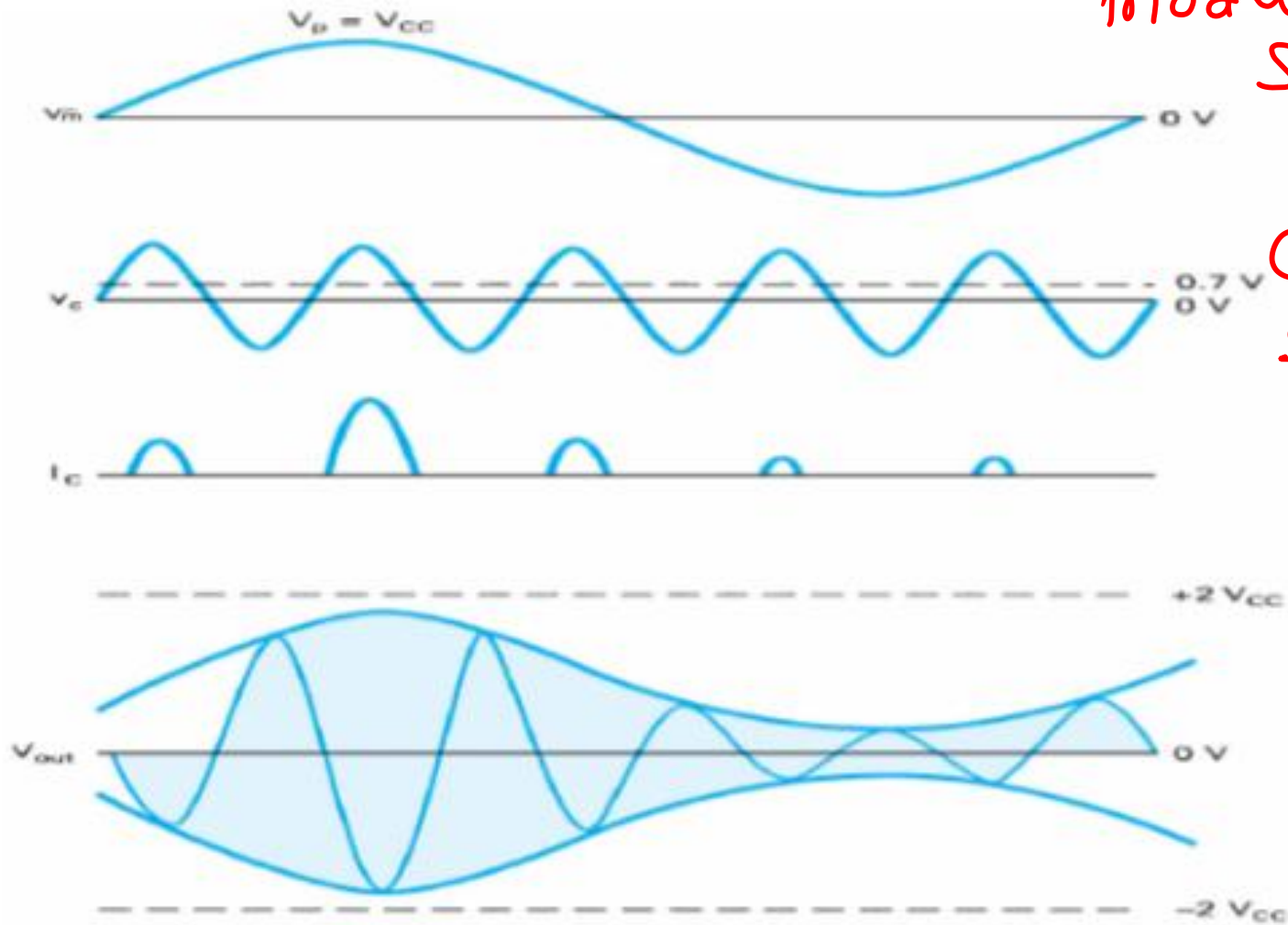

modulating
Signal

Carrier
Signal

Max

min

Comparison of Emitter and Collector Modulator

Emitter modulator	Collector modulator
• Less symmetrical envelope • Less power efficiency • Low output power • Require only small modulating signal drive power • Simpler circuit	• More symmetrical envelope • Higher power efficiency • Higher output power • Need higher amplitude modulating signal • Complex circuit