



K. J. Somaiya School of Engineering

Batch: A2 Roll No.: 1601032401 44
Experiment / assignment / tutorial No. 06
Grade: AA / AB / BB / BC / CC / CD / DD

Signature of the Staff In-charge with date

TITLE: OP-AMP Linear Applications


AIM: To analyse and design adder circuits using OP-AMP

OUTCOME: Students will be able to understand the basics of analog Integrated circuits.

PROCEDURE:

1. Assemble OPAMP circuits as shown in diagram 1.
2. Analyse the circuit with reference to observation table I.
3. Apply two DC signals of different amplitudes and find the output voltage and comment.
4. In the second part, design an adder circuit as per the given input output relationship.
5. Repeat step 2 (use observation table II) and step 3 for the designed circuit.

Circuit Diagram 1: Op Amp as Subtractor

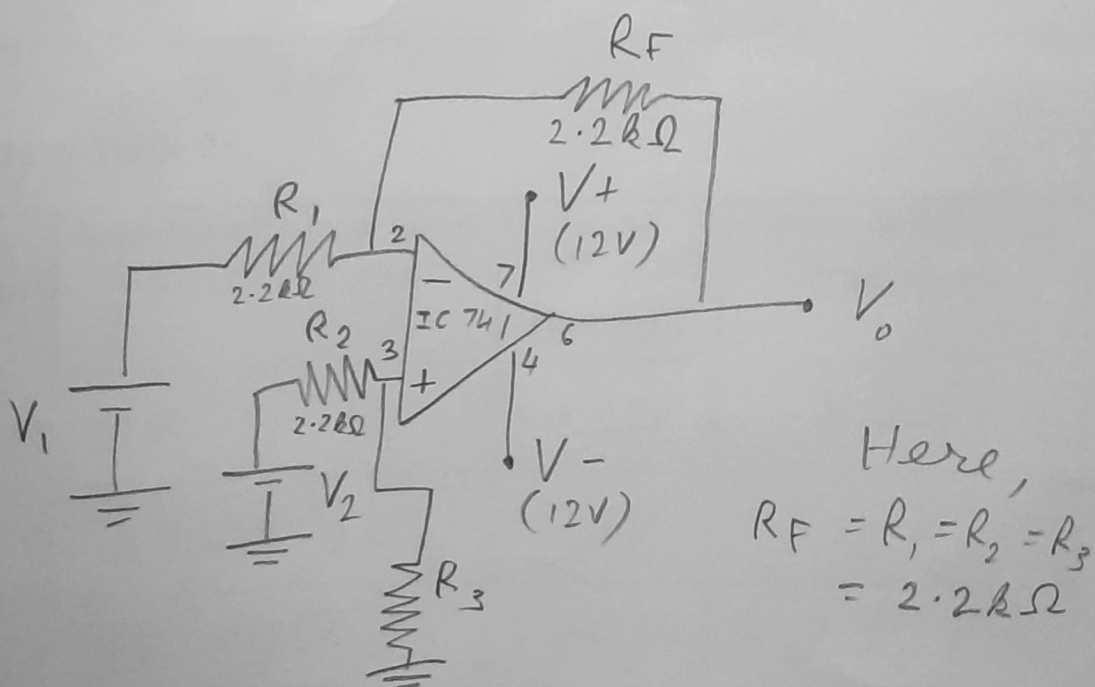



K. J. Somaiya School of Engineering


Observation Table 1:

Sr. No	Input Signal (V ₁)	Input Signal (V ₂)	Output Voltage (V _o) (Practical)	Output Voltage (V _o ') (Theoretical)
1.	1V	15V	11.1V (vs sat)	14V
2.	1V	10V	8.9V	9V
3.	2V	6V	4.01V	4V
4.	6V	2V	-4.015V	-4V
5.	5V	3V	-2.02V	-2V



Circuit Diagram 2: Op Amp as Adder

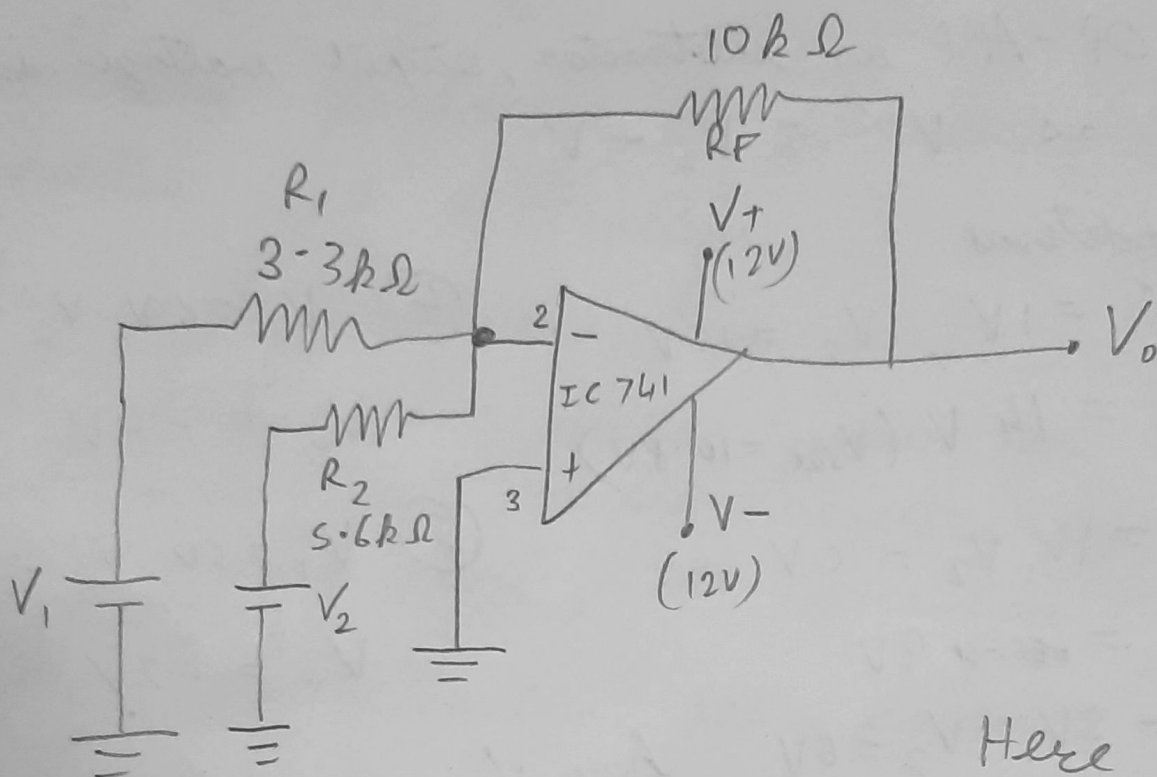➤ Design circuit for $V_o = -(2V_1 + V_2)$ $-(3V_1 + 2V_2)$



Here,
 $\frac{R_F}{R_1} = 3$
 $\frac{R_F}{R_2} = 2$

Observation Table 2:

Sr. No	Input Signal (V ₁)	Input Signal (V ₂)	Output Voltage (V _o) (Practical)	Output Voltage (V _o ') (Theoretical)
1.	1V	1V	-4.95V	-4.78V
2.	2V	2V	-9.8V	-9.56V
3.	1V	2V	-7.9V	-7.78V
4.	1V	3V	-9.3V	-8.84V
5.	-	-	-	-

**Theoretical Calculations:****I) For Op Amp as Subtractor:**

→ For OP-AMP as subtractor, output voltage is given as $V_o' = V_2 - V_1$

For conditions

① $V_1 = 1V, V_2 = 15V$

② $V_o = 14V (V_{sat} = 10.8V)$

③ $V_1 = 1V, V_2 = 10V$

$V_o = 9V$

④ $V_1 = 2V, V_2 = 6V$

$V_o = 4V$

⑤ $V_1 = 6V, V_2 = 2V$

$V_o = -4V$

⑥ $V_1 = 5V, V_2 = 3V$

$V_o = -2V$

here, $V_{sat} = \pm 90\% V_{cc}$

$= \pm \frac{90 \times 12}{100} = 10.8V$

II) For Op Amp as Adder:

→ We have designed for following condⁿ:-
 $V_o' = -(3V_1 + 2V_2)$

Comparing with eqⁿ:- $V_o = -\left[\frac{R_F}{R_1} V_1 + \frac{R_F}{R_2} V_2\right]$

$R_1 = 3.3k\Omega$

$R_2 = 5.6k\Omega$ (As per lab)

→ $\frac{R_F}{R_1} = 3 \quad \left| \quad \frac{R_F}{R_2} = 2\right.$

∴ Take $R_F = 10k\Omega$

For Condⁿ to satisfy

$V_1 = 1V, V_2 = 1V$

$V_o = -(3 \times 1 + 5.6 \times 1)$
 $= -4.78$

$V_1 = 1V, V_2 = 3V$

$V_o = -(3 \times 1 + 5.6 \times 3)$
 $= -8.89V$

$V_1 = 1V, V_2 = 2V$

$V_o = -(3 \times 1 + 5.6 \times 2)$
 $= -7.78V$

$V_1 = 2V, V_2 = 2V$

$V_o = -(3 \times 2 + 5.6 \times 2)$
 $= -9.56V$



Conclusion: So by this experiment, We were able to say that using IC-741 OP-AMP correctly performs ~~to~~ process like addition and subtraction.

As ~~a~~ subtraction, We used $2.2k\Omega$. For addition we were given the equation and we used same resistor by choice and carried out the operation.

The results were near correct