

DLD (SY EXTC) (Sem III)

July - Oct. 2025

ISE paper solution & marking scheme

Q.1a) 1) $(7)_8 - (4)_8$ using 2's complement method.

$$(7)_8 = (111)_2 \quad 111 \quad 1m$$

$$(4)_8 = (100)_2 \quad - 100$$

1's complement of 100 is 011

$$2's \text{ complement of } 100 \text{ is } \begin{array}{r} 011 \\ + 1 \\ \hline 100 \end{array} \quad 1/2m$$

$$\therefore \begin{array}{r} 111 \\ + 100 \\ \hline 1011 \end{array}$$

end around carry

Answer is $(011)_2$

$$(011)_2 = (3)_8$$

1m.

2) Convert $(2A5)_H$ into decimal, octal & BCD

$$(2A5)_H = (677)_{10} \quad (1m)$$

$$(2A5)_H = \underline{001010100101}$$

$$(2A5)_H = (1245)_8 \quad (1m)$$

$$(2A5)_H = (677)_{10} \quad (1/2m)$$

$$6 = 0110$$

$$7 = 0111$$

$$7 = 0111$$


$\therefore$ BCD of $(2A5)_H$ is 011001110111

3) Gray to binary code $(1 1/2m)$

$$\begin{array}{r} 10110 \\ 9493929190 \\ \downarrow \downarrow \downarrow \downarrow \downarrow \\ 10110 \\ 11011 \\ b_4 \ b_3 \ b_2 \ b_1 \ b_0 \end{array}$$

Binary code of 10110 Gray code is $\boxed{11011}$

ckt implementation dia.

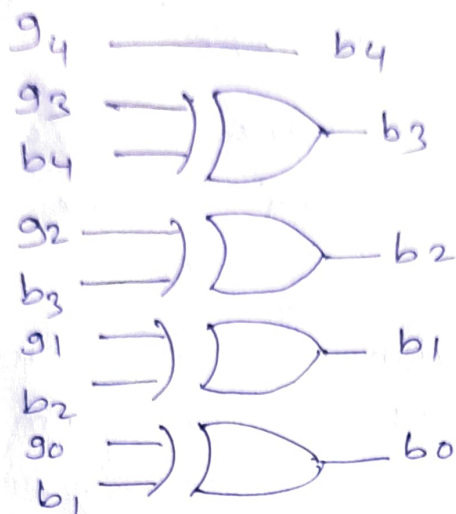

(1m)

4) BCD addition of $(9)_{10} + (5)_{10}$

BCD of $(9)_{10} \rightarrow 1001$
BCD of $(5)_{10} \rightarrow 0101$ } (1m) $(9)_{10} + (5)_{10} = (14)_{10}$

$$\begin{array}{r} 1001 \\ + 0101 \\ \hline \end{array}$$

$1110 \leftarrow$ Invalid BCD - (1m)

$$+ 0110$$

$10100 \leftarrow$ Valid BCD. (12m)

Answer is (00010100) BCD

1(b) Diagram of 4 bit controlled binary adder/subtractor - (5m)

Q. 2(a) 1) $F(a, b, c) = \sum m(0, 2, 4, 6, 7)$

	bc	00	01	11	10
a	0	0	1	1	0
1	0	1	0	0	1

$$= c \cdot (\bar{a} + \bar{b}) \quad (1m)$$


2) $F(p, q, r) = \sum m(0, 1, 3, 5)$

	qr	00	01	11	10
p	0	1	1	1	0
1	0	1	0	1	0

$$= \bar{p} \cdot \bar{q} + \bar{p}r + \bar{q}r \quad (1m)$$

(11/2m)


$$Y = \sum m(1, 3, 7, 11, 15) + d(0, 2, 5)$$

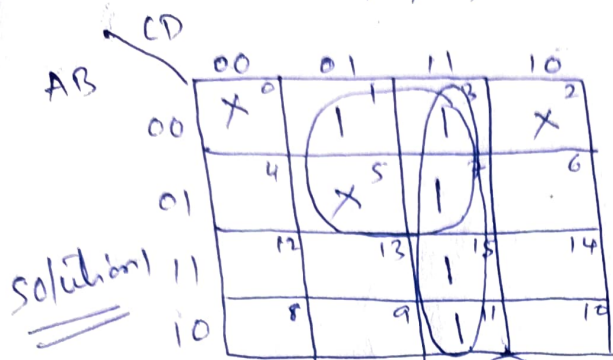

Solution 1

$2 \frac{1}{2} m$

$$Y = \overline{A}D + CD$$

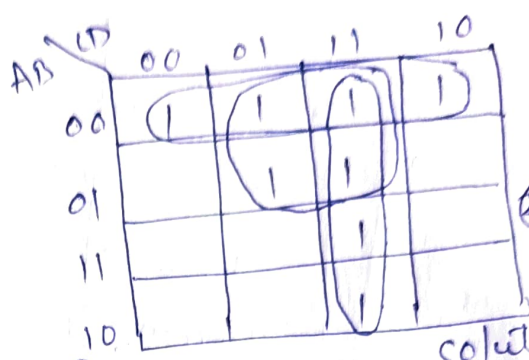

Solution 2

OR


$$Y = \overline{A}\overline{B} + \overline{A}D + CD$$

$2 \frac{1}{2} m$

Q. 2(b) $Y = F(A, B, C, D) = \sum m(0, 2, 3, 4, 8, 9, 12, 14, 15)$

1) Using single 16:1 Mux

2) Using single 8:1 mux

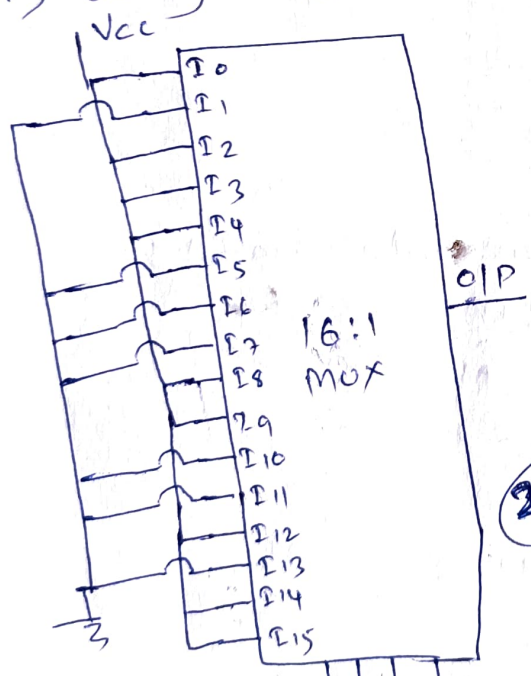


$2 m$

ΣPS				O/P
A	B	C	D	Y
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	0
1	0	1	1	0
1	1	0	0	1
1	1	0	1	0
1	1	1	0	1
1	1	1	1	1

- $I_0 = \overline{D}$
- $I_1 = 1$
- $I_2 = \overline{D}$
- $I_3 = 0$
- $I_4 = 1$
- $I_5 = 0$
- $I_6 = \overline{D}$
- $I_7 = 1$


$2 m$

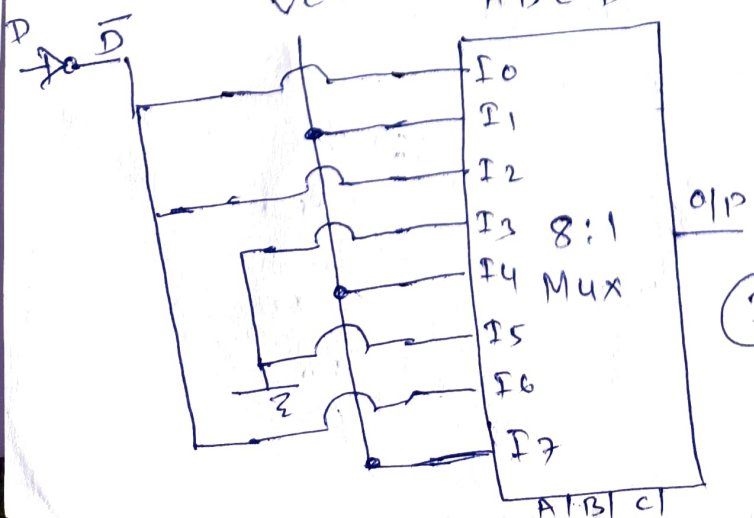

$3 m$



③ Using 1:16 Demux

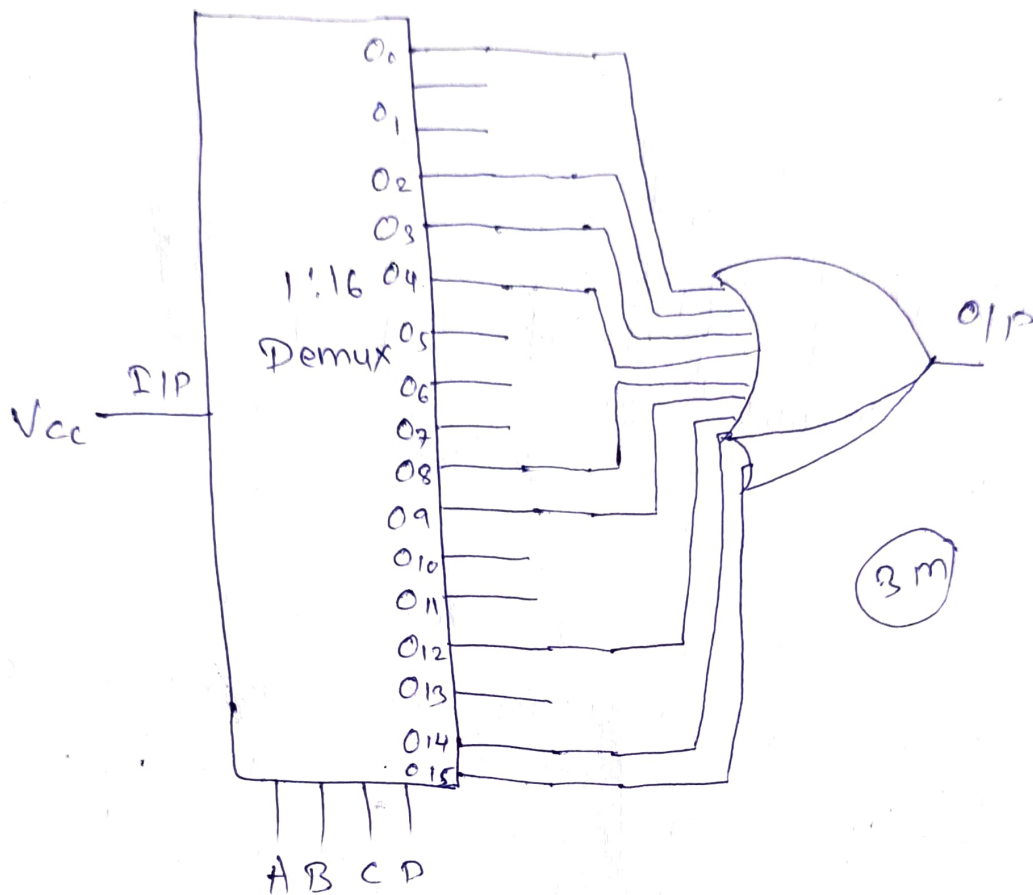

Q.3

SR FF using NOR gate dia - 1m

Truth table - 1m

Working - 3M

OR

Diagram of JK FF with - 1m

-ve edge clock

Truth table - 1m

Working - 3M.