

Analog Electronics

Frequency Response of BJT & MOSFET Amp.

Integrated ckt. biasing techniques

M3 • Fundamentals of op. Amp. (& Applications)

M4 • Applications of Power Amp.


M5 • Oscillators

Basic Concepts

* Frequency Response



- 1) Voltage gain
 - 2) i/p & o/p
 - 3) Current gain
 - 4) o/p & i/p
- assumed measurements for mid-frequency range.

Freq. Ranges: Low, Mid, High

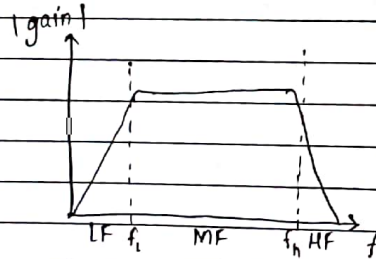


The parameters above are measured only for MF.
Bandwidth = $f_H - f_L$

* Frequency Range

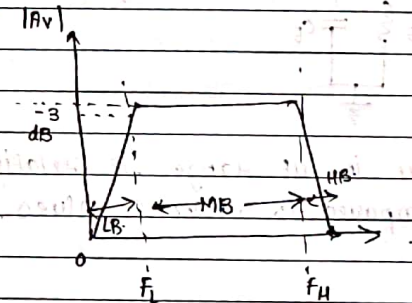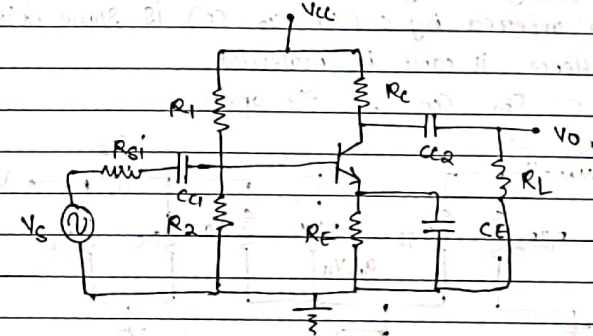

In MF Range:
to calculate $A_{v \text{ mid}}$
(we did AC analysis
where all C were
shorted) & DC
supply was grounded
 C_{c1}, C_{c2} : coupling C
 C_E : Bypass C

* Hybrid π model: (MF)

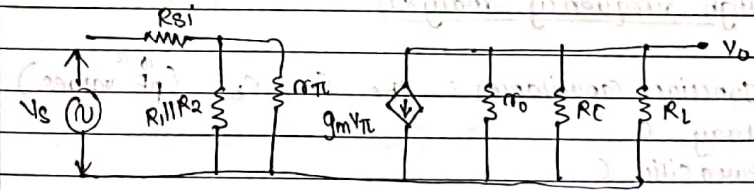


$$A_v = -g_m (R_C \parallel R_L \parallel R_o)$$

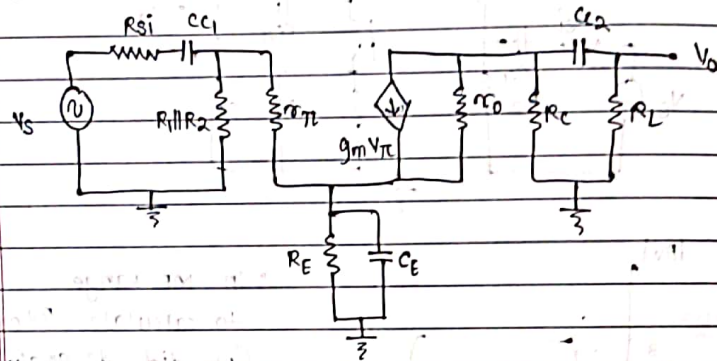g) Effects of c on gain:

* Low frequency Analysis:

- Reactance offered by c (c_1, c_2, c_E) is some finite value. Hence, it can't be neglected.
- Junction C: $c_{be}, c_{ce}, c_{bc} \rightarrow$ open.



$\rightarrow c_1, c_2$ and c_E are in μF ranges, i.e. relatively high C-value, compared to other C-values.

$$\text{and, } X_c = \frac{1}{2\pi f \cdot C}$$


$\rightarrow$ combined effect of c_1, c_2 & c_E reduces gain, $\therefore$ they offer a finite reactance value to the i/p & o/p signal.

* High frequency Analysis:

- Junction Capacitances: c_{be}, c_{ce}, c_{bc} (10^{-12} pF values)
- Stray C
- Parasitic C


For MF analysis, these junction C are assumed to be open bcz X_c tends to ∞ . $\therefore$ for HF, X_c offered by these junction C can't be neglected.

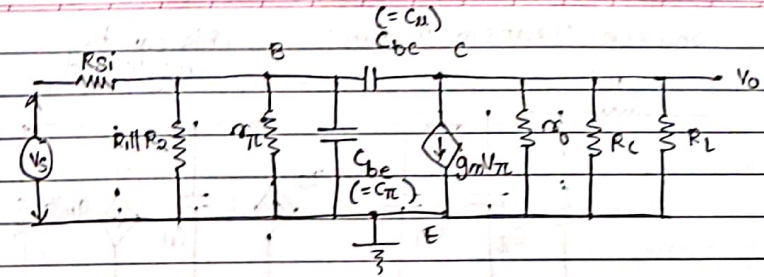- $c_1, c_2, c_E \rightarrow$ shorted
- c_{ce} is very very small



* Miller's Theorem:

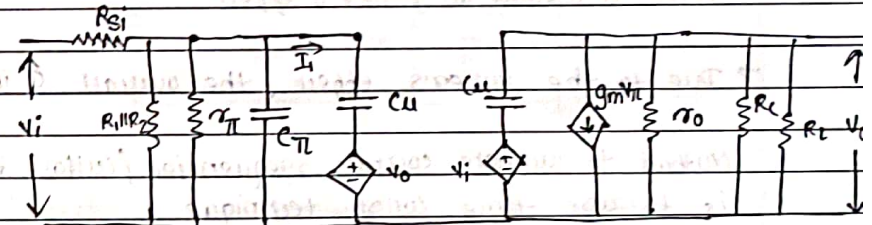- If it is a 2 port Network, then acd. to theorem the element connecting i/p & o/p is divided in 2 parts: a) i/p & ground (connected betn.) b) o/p & ground (—, —)



$$\rightarrow I_1 = \frac{V_i - V_o}{1/j\omega C_u}$$

$$\cdot \text{ here, } V_o = -g_m V_\pi (r_o)$$

$$\therefore I_1 = j\omega [C_u [1 + g_m (r_o \parallel R_c)]] V_\pi$$


$$\therefore I_1 = \frac{V_\pi}{1/j\omega C'} \quad C' = C_u [1 + g_m (r_o \parallel R_c)]$$

$$\cdot \text{ here, } C_m = C' = C_u [1 + g_m (r_o \parallel R_c)]$$

$$\text{(Miller's Capacitance)}$$

$$\therefore C_m = C_u [1 + |A_v|_{mid}]$$

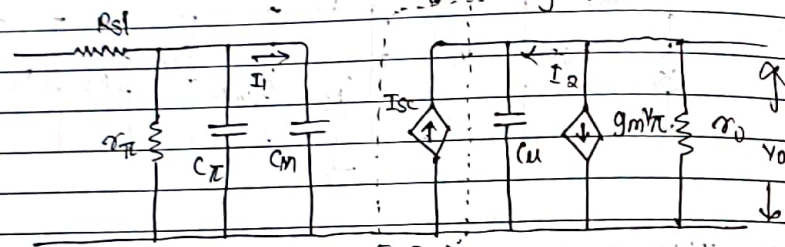- Source Transformation: this can be neglected



→ Applying Miller's Thm, the C_u is getting multiplied by the term $(1 + |A_{v_{mid}}|)$ due to which the overall C_u value is ~~not~~ increased, and this is Miller's capacitance, and the multiplication effect is termed as Miller's effect.

→ Due to the Miller's effect, the overall C increases

- Method to calculate corner frequencies / cutoff freq. is to use time const. technique.

$$F = \frac{1}{2\pi\tau}$$

here τ : time const. of circuit

$$(\tau = R_{eq} C_{eq})$$

Now,

$$f_{H_{CT}} = \frac{1}{2\pi \cdot C_{eq} R_{eq}}$$

$$C_{eq} = C_{\pi} + C_m$$

∴ overall $C \uparrow$, Higher cutoff freq. $\downarrow$ after apply Miller's Thm.


- Due to Miller's effect, $C_{overall} \uparrow$, $f_H \downarrow$ ∴ at const. f_L , BW. $\downarrow$, i.e. Miller's effect reduces Band width.

* CE - Bypass


- Q] For a CE bypass V-divider bias BJT amp. determine MF. voltage gain, 3dB f_L , 3dB f_H and BW. given that C_{C1} , C_{C2} and C_E along with C_{π} & C_u (μF) (pF)

- For Mid Band A_v calculation (DC analysis & AC-MF analysis)
- To calculate f_L (low F. analysis), f_H (HF. analysis)

→ Diagram:

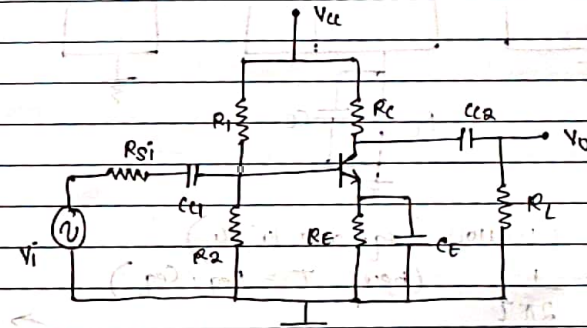

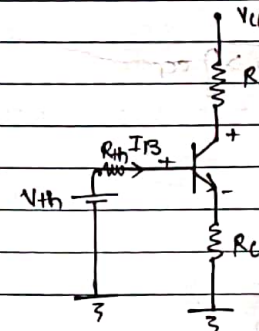(*) Equivalent DC-Thevenin's ckt and DC Analysis



$$V_{th} = \frac{V_{cc} \cdot R_2}{R_1 + R_2}$$

• Now, KVL on i/p loop:

$$a) I_B = \frac{V_{th} - V_{BE}}{R_{th} + (1 + \beta) R_E}$$

$$b) I_C = \beta I_B$$


c) calculate V_{CE} only when Q-point

→ Now, $g_m = \frac{I_C}{V_T}$, $r_o = \frac{V_A}{I_C}$, $r_{\pi} = \frac{\beta V_T}{I_C}$ (If $V_A \neq \infty$)

(2) MF AC analysis

$$A_{v \text{ mid}} = -g_m (R_c \parallel R_L \parallel r_o)$$

(3) LF Analysis:

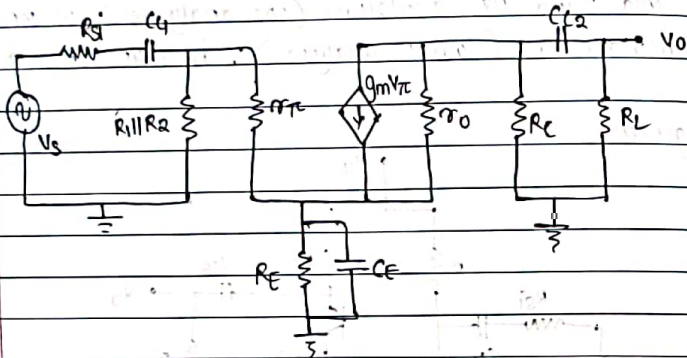

a) $\rightarrow f_{L_{C1}}$ (1-cutoff freq. due to C_1)

$$= \frac{1}{2\pi \tau} \quad (\text{here } \tau = R_{eq} \cdot C_{eq})$$

Now, $R_{eq} = R_{si} + (R_1 \parallel R_2 \parallel [r_{\pi} + (1+\beta)R_E])$ $\rightarrow$ UNBYPASS

$C_{eq} = C_1 \rightarrow R_{si} + (R_1 \parallel R_2 \parallel r_{\pi})$ $\rightarrow$ BYPASS

$$\therefore f_{L_{C1}} = \frac{1}{2\pi [R_{si} \parallel R_1 \parallel R_2 \parallel (r_{\pi} + (1+\beta)R_E)] C_1}$$

b) $\rightarrow f_{L_{C2}}$

$$R_{eq} = R_c + R_L$$

$$C_{eq} = C_2$$

$$\therefore f_{L_{C2}} = \frac{1}{2\pi [R_c + R_L] C_2}$$

c) $\rightarrow f_{L_{CE}}$


$$R_{eq} = R_E \parallel \left(\frac{R_{si} \parallel R_1 \parallel R_2 + r_{\pi}}{1+\beta} \right)$$

$$C_{eq} = C_E$$

$$\therefore f_{L_{CE}} = \frac{1}{2\pi [R_E \parallel \left(\frac{R_{si} \parallel R_1 \parallel R_2 + r_{\pi}}{1+\beta} \right)] C_E}$$

Largest of 3 is f_L

(4) HF Analysis:

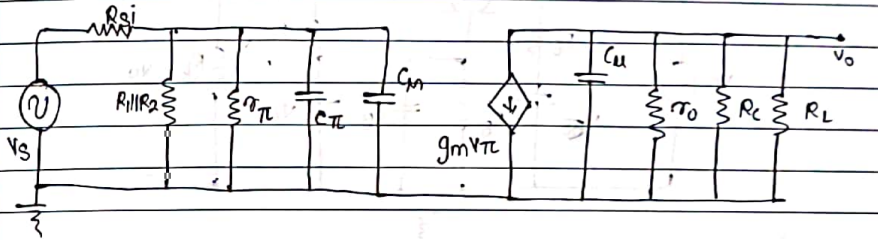

a) $\rightarrow f_{H_{C1}} = \frac{1}{2\pi [R_{si} \parallel R_1 \parallel R_2 \parallel r_{\pi}] (C_{\pi} + C_m)}$

here,

$$C_m = C_{\mu} [1 + |A_{v \text{ mid}}|]$$


b) $\rightarrow f_{H_{C2}} = \frac{1}{2\pi [r_o \parallel R_c \parallel R_L] C_{\mu}}$

— (Smallest of 2 is f_H) —


$\rightarrow$ Now,

$$BW = f_H - f_L$$

* CB - BJT Amp:

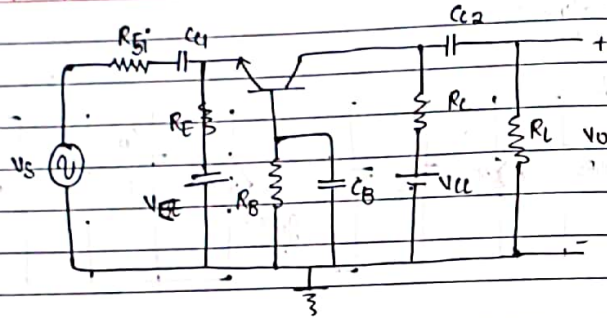

→ DC Analysis:

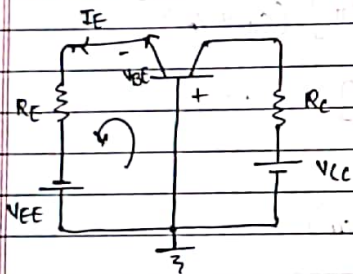

• KVL on i/p side

$$\therefore -V_{BE} - I_E R_E + V_{EE} = 0$$

$$\therefore I_E = \frac{V_{EE} - V_{BE}}{R_E}$$

Now,



$$I_B = \frac{I_E}{1 + \beta}$$

$$I_C = \beta I_B$$


$$\text{and } g_m = \frac{I_C}{V_T} \rightarrow r_{\pi} = \frac{\beta V_T}{I_C}$$

$$\rightarrow r_o = \frac{V_A}{I_C}$$

→ LF Analysis:

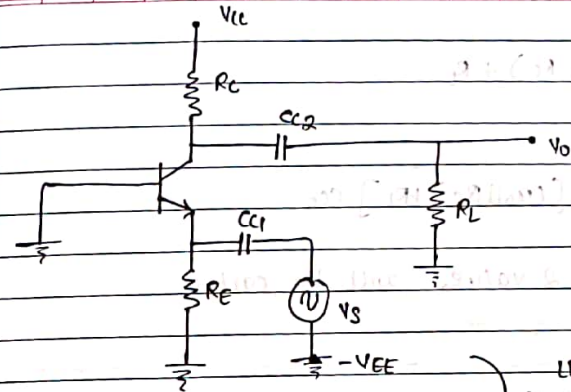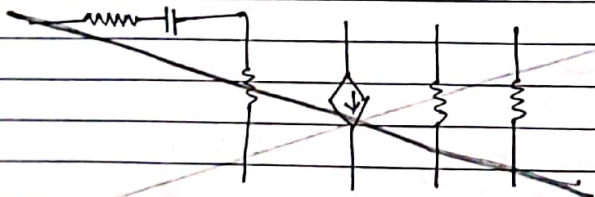

LF Hybrid π model

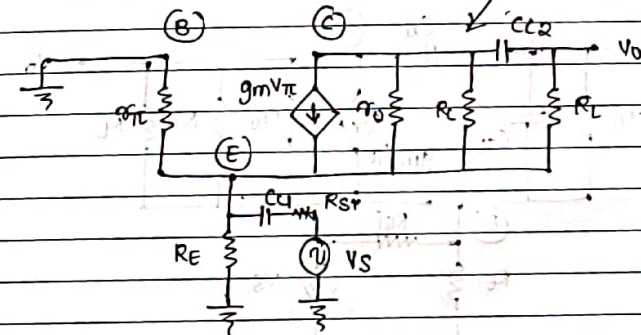

$$a) f_{L_{C_{C1}}} = \frac{1}{2\pi \tau}$$

$$R_{eq} = R_{S1} + \left[R_E \parallel \frac{r_{\pi}}{1 + \beta} \right]$$

$$C_{eq} = C_{C1}$$


$$\therefore f_{L_{C_{C1}}} = \frac{1}{2\pi \left[R_{S1} + \left(R_E \parallel \frac{r_{\pi}}{1 + \beta} \right) \right] C_{C1}}$$

b) $f_{L_{u2}}$:
 $R_{eq} = (r_o \parallel R_c) + R_L$

$\therefore f_{L_{u2}} = \frac{1}{2\pi [(r_o \parallel R_c) + R_L] C_{C2}}$


- Largest of 2 values will be called as 3dB f_L .

→ HF Analysis

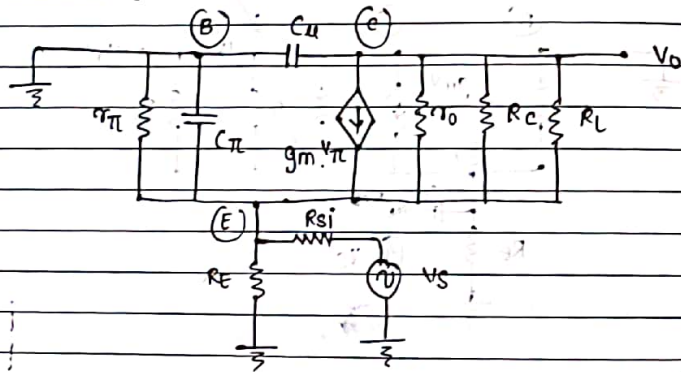

- Applying Miller's Thm. :

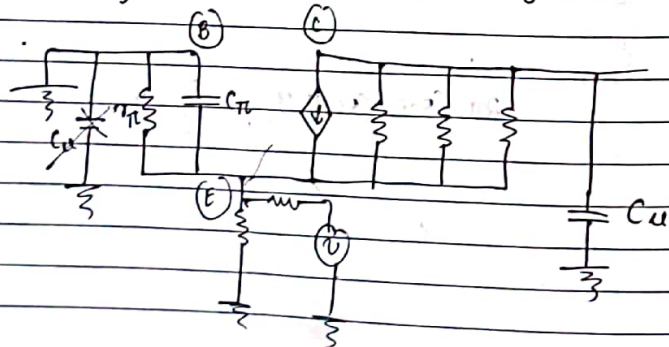Replacing the C_u (cap.) betn. (Base) & (C) with
 i) C_u (cap.) betn. (B) and ground.
 ii) C_u (cap.) betn. (C) and ground.



- at the i/p side C_u is connected betn. (B) and ground but (B) itself is grounded $\therefore C_u$ becomes redundant, $\therefore C_u$ is to be neglected.

This signifies,

Hence there is no Miller effect, $\therefore C_{eq}$ decreases and hence, BW $\uparrow$.

→ This concludes, BW offered in CB $>$ BW in CE config.
 Reason: No Miller's effect.


• $f_{H_i} = \frac{1}{2\pi [R_{Si} \parallel R_E \parallel \frac{r_{\pi}}{1+\beta}] C_{\pi}}$

• $f_{H_o} = \frac{1}{2\pi [r_o \parallel R_c \parallel R_L] C_u}$

→ Mid freq. Analysis:

$|A_v|_{mid} = g_m (r_o \parallel R_c \parallel R_L)$

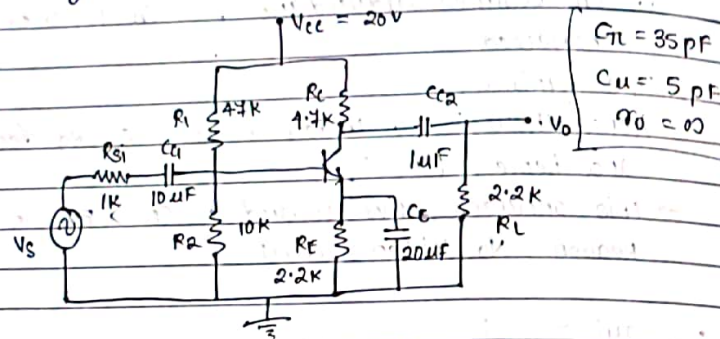- q] Determine the upper, lower f_c , calculate BW. for the ckt. given, also calculate gain-BW product.




→ Solution:

A) DC Analysis:

Now,

$$R_{th} = \frac{R_1 R_2}{R_1 + R_2} = \frac{(47)(10)}{57} (10^3) = 8.24 \text{ K}\Omega$$
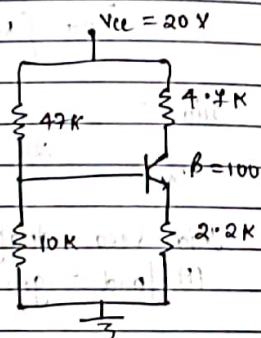
$$V_{th} = V_{cc} \frac{R_2}{R_1 + R_2} = \frac{(20)(10)}{57} (10^3) = 3.5 \text{ V}$$




$$V_{th} - I_B R_{th} - V_{BE} - R_E I_E = 0$$

$$\therefore 3.5 - I_B (8.24)(10^3) - 0.7 - (2.2)(10^3)(100+1)I_B = 0$$

$$\therefore I_B = 12.2 \text{ }\mu\text{A}$$

$$\therefore I_C = 1.22 \text{ mA} = \beta I_B$$
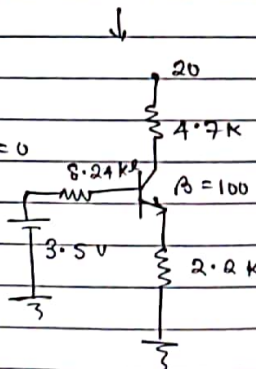
$$g_m = \frac{I_C}{V_T} = \frac{1.22 (10^{-3})}{26 (10^{-3})} = 46.9 \text{ mS}$$



$$\begin{aligned} r_{\pi} &= \frac{\beta V_T}{I_C} = \frac{(100)(26)(10^{-3})}{1.22 (10^{-3})} \\ &= 2131.14 \text{ }\Omega \\ &= 2.13 \text{ K}\Omega \end{aligned}$$

B) AC Analysis:

$$\begin{aligned} A_{v \text{ mid}} &= -g_m [R_C \parallel R_L \parallel r_o] \\ &= -(46.9)(10^{-3}) [4.7(10^3) \parallel 2.2(10^3)] \\ &= -70.2 \end{aligned}$$

$$\begin{aligned} \text{HP Analy. } A_{v s \text{ mid}} &= -g_m (R_C \parallel R_L \parallel r_o) \left[\frac{R_B \parallel r_{\pi}}{R_B \parallel r_{\pi} + R_{S1}} \right] \\ &= -(46.9)(10^{-3}) [1.49(10^3)] \left[\frac{1.69(10^3)}{1.69(10^3) + 1(10^3)} \right] \\ &= -44.10 \end{aligned}$$

C) IF Analysis:

$$\begin{aligned} a) f_{L1} &= \frac{1}{2\pi [r_{\pi} \parallel R_1 \parallel R_2 + R_{S1}] (10)(10^{-6})} \\ &= \frac{1}{2\pi [(2.13 \text{ K} \parallel 47 \text{ K} \parallel 10 \text{ K}) + 1 \text{ K}] (10)(10^{-6})} \\ &= \frac{1}{2\pi (2.69)(10)(10^{-6})(10^3)} \\ &= 5.9 \text{ Hz} \end{aligned}$$

$$b) f_{L2} = \frac{1}{2\pi (R_C + R_L) C_{C2}} = 23 \text{ Hz}$$

$$\begin{aligned} c) f_{H1} &= \frac{1}{2\pi [R_E \parallel (\frac{R_C + r_o}{1+\beta} \parallel R_1 \parallel R_2)]} \\ &= \frac{1}{2\pi [2.2(10^3) \parallel (2.13(10^3) + \frac{1(10^3) \parallel 47 \text{ K} \parallel 10 \text{ K}}{101})]} \end{aligned}$$

D) HF Analysis:

$$f_{hi} = \frac{1}{2\pi (\tau_{\pi} \parallel R_1 \parallel R_2 \parallel R_{Si}) (\tau_{\pi} + m)}$$

here, $m = (1 + A_{VSMid})$


$$\therefore m = 5(10^{10}) [-43.1]$$

$$= 215.5 \text{ pF}$$

$$\therefore f_{hi} = \frac{1}{2\pi [2.13 \text{ K} \parallel 147 \text{ K} \parallel 10 \text{ K} \parallel 1 \text{ K}] (215.5)(10^{-12})}$$

$$= \frac{1}{2\pi [2.03 \text{ K} \parallel 0.909 \text{ K}] [(215.5)(10^{-12}) + 35]}$$
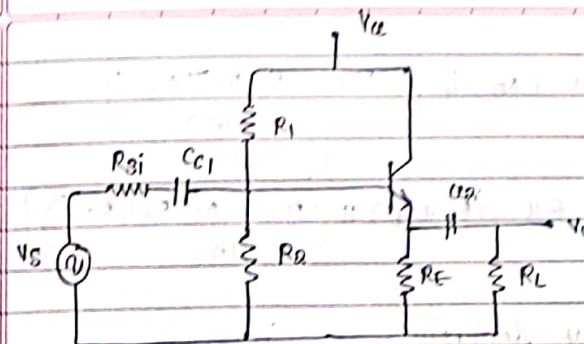
$$= \frac{1}{2\pi (0.628)(10^3)(215.5)(10^{-12}) + 35}$$




• DC Analysis
is same as
CE-BJT amp.

→ MF AC Analysis:

$$A_V = \frac{(1+\beta)(R_{\pi} \parallel R_E)}{R_{\pi} + (1+\beta)(R_{\pi} \parallel R_E)} \approx 1$$

→ LF Analysis:

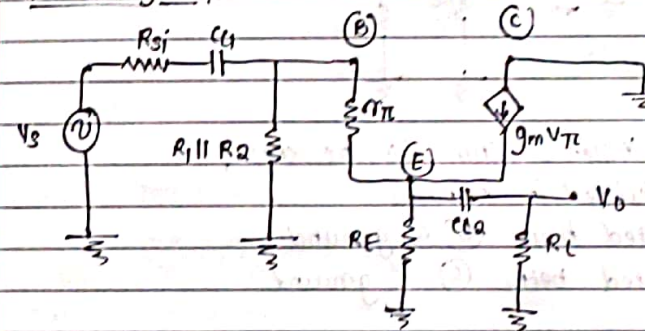


$$f_{LCL} = \frac{1}{2\pi \cdot R_{eq} \cdot (C_{C1})}$$

$$\text{Now, } R_{eq} = R_{Si} + [R_1 \parallel R_2 \parallel (\tau_{\pi} + (R_E \parallel R_C)(1+\beta))]$$

$$\therefore f_{LCL} = \frac{1}{2\pi [R_{Si} + (R_1 \parallel R_2 \parallel (\tau_{\pi} + (R_E \parallel R_C)(1+\beta)))] C_{C1}}$$



$f_{low} :$
 $R_{eq} = R_L + R_E \parallel \left[\frac{r_{\pi} + R_1 \parallel R_2 \parallel R_{Si}}{(1+A)} \right]$
 $\therefore f_{low} = \frac{1}{2\pi (R_L + R_E \parallel \left[\frac{r_{\pi} + R_1 \parallel R_2 \parallel R_{Si}}{(1+A)} \right]) C_0}$

→ High Frequency Analysis :

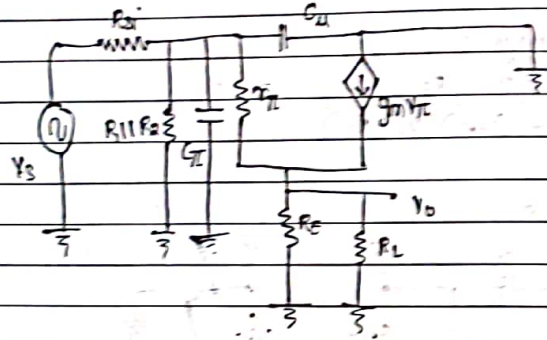

• Applying Miller's Thm. to the ckt.
 C_C is divided in 2 parts:

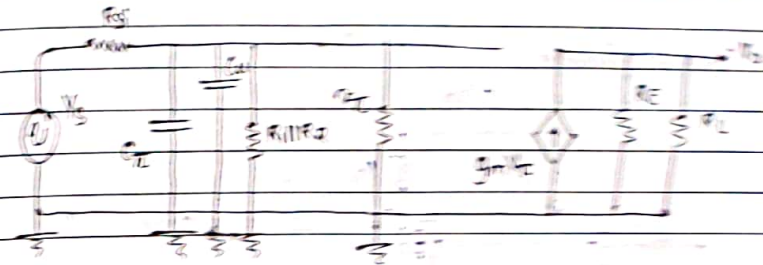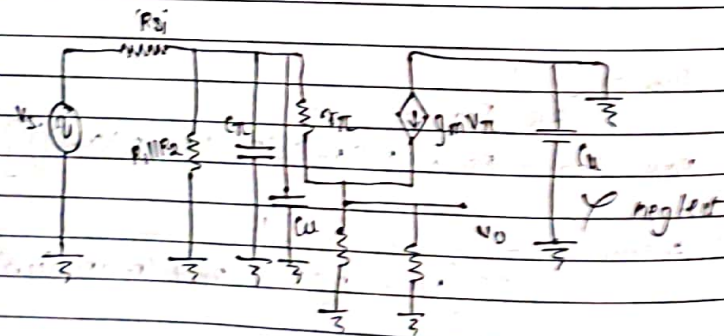- C_C connected betn. (B) & ground.
- C_C connected betn. (C) & ground.



$f_{hi} = \frac{1}{2\pi [R_{Si} \parallel R_1 \parallel R_2 \parallel R_E \parallel R_L (1+g_m R_E')] [C_C + \frac{C_C}{1+g_m R_E'}]}$


→ CC - configuration :

- There is no Miller effect at the output and the capacitance at the side (C_C) is reduced by $(1+g_m R_E')$. In parallel C_C is less as compared to CE - config. Hence, we say: BW of CC - config is largest of the three.
- No Miller's effect on V_{in} & V_{out} .


$\text{Gain} = (C_E = C_B), (C_C \text{ - unity})$
 $BW : C_E < C_B < C_C$

MOSFET Amplifier Frequency Response

A) Common Source:

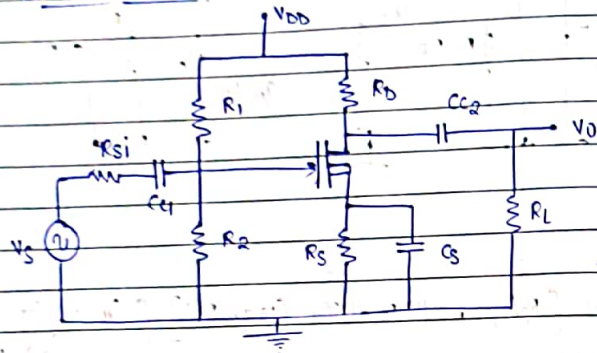

* DC Analysis

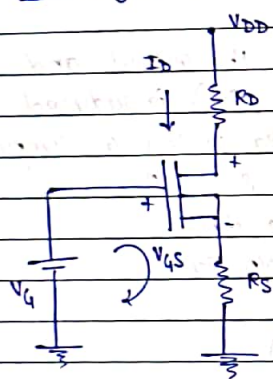

$$V_G = \frac{V_{DD} \cdot R_2}{R_1 + R_2}$$

• NOW,

$$V_G - V_{GS} - I_D R_S = 0$$

$$\therefore V_G = V_{GS} + I_D R_S$$

• NOW,

$$I_D = K_n [V_{GS} - V_{TN}]^2$$


* Parameters:

$$g_m = 2K_n [V_{GS} - V_{TN}]$$

* Mid-frequency Analysis:

- $(A_v)_{mid} = -g_m [r_d \parallel R_D \parallel R_L]$
- $(A_{v_s})_{mid} = -g_m [r_d \parallel R_D \parallel R_L] \frac{(R_1 \parallel R_2)}{(R_1 \parallel R_2) + R_{Si}}$

* LF Analysis:

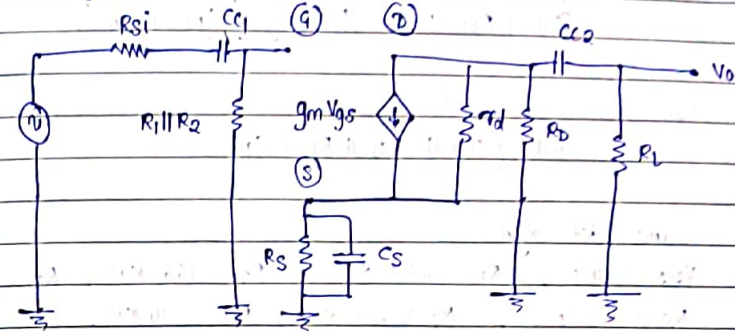


$$f_{L_{C_{\pi}}} = \frac{1}{2\pi [R_{Si} + R_{th}] C_{\pi}}$$

$$f_{L_{C_L}} = \frac{1}{2\pi [R_D + R_L] C_L}$$

$$f_{L_{C_S}} = \frac{1}{2\pi [R_S \parallel 1/g_m] C_S} \quad \because 1/g_m \ll (R_D \parallel R_L)$$

→ R offered by $(g_m V_{gs})$ source is always $= 1/g_m$

* HF Analysis:

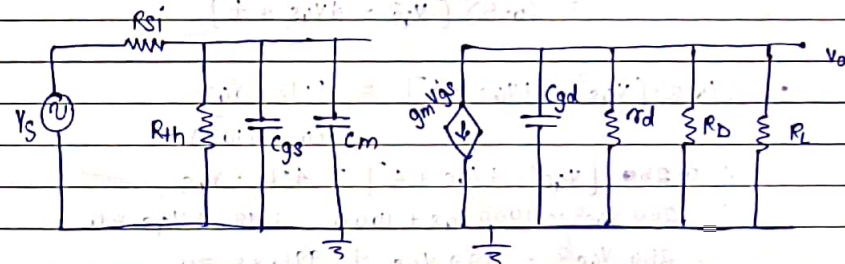

$$\text{here, } C_m = C_{gd} [1 + |A_{v_{mid}}|]$$

$$f_{hi} = \frac{1}{2\pi [R_{si} \parallel R_1 \parallel R_2] [C_{gs} + C_m]}$$

$$f_{uo} = \frac{1}{2\pi [r_d \parallel R_D \parallel R_1] C_{gd}}$$

g) Same ckt dgm.

- $V_{DD} = 10V$, $R_1 = 234 K\Omega$, $R_2 = 166 K\Omega$, $R_D = 9 K\Omega$,
 $R_S = 0.5 K\Omega$, $R_L = 20 K\Omega$, $R_{si} = 10 K\Omega$.
 - $k_n = 0.5 mA/V^2$, $V_{TN} = 2V$, $\lambda = 0$, $C_{gs} = 1 pF$,
 $C_{gd} = 0.1 pF$, $C_{c1} = C_{c2} = 1 \mu F$, $C_S = 10 \mu F$.
- Calculate: BW of CS amplifier.

→ Solution:

→ DC Analysis:

$$V_G = \frac{10(166)(10^3)}{(234+166)K} = 4.15 V$$

Now,

$$I_D = \frac{V_G - V_{GS}}{R_S} = \frac{4.15 - V_{GS}}{0.5(10^3)}$$

$$\text{also, } I_D = (0.5) \left[\frac{(V_{GS} - 2)^2}{10^3} \right]$$

$$= (0.5) [V_{GS}^2 - 4V_{GS} + 4]$$

$$(0.5) [V_{GS}^2 - 4V_{GS} + 4] = \frac{4.15 - V_{GS}}{(0.5)(10^3)}$$

$$\therefore 0.25 [V_{GS}^2 - 4V_{GS} + 4] = 4.15 - V_{GS}$$

$$\therefore 250 V_{GS}^2 - 1000 V_{GS} + 1000 - 4.15 + V_{GS} = 0$$

$$\therefore 250 V_{GS}^2 - 999 V_{GS} + 995.85 = 0$$

$$V_{GS} = 2.1 V, 1.9 V$$

When, $V_{GS} = 2.1$

$$I_D = (0.5)(0.1)^2$$

$$= 5 mA$$

$$V_{GS} = 1.9$$

$$I_D = (0.5)(-0.1)^2$$

$$= 5 mA$$

$$\therefore 0.25 V_{GS}^2 - V_{GS} + 1 = 4.15 - V_{GS}$$

$$\therefore 0.25 V_{GS}^2 - 3.15 = 0$$



$$\therefore V_{GS} = \pm 3.51$$

When, $V_{GS} = 3.91$

$$\therefore I_D = (0.5)(-1.18 mA)$$




* Common Gate MOSFET Amplifier:

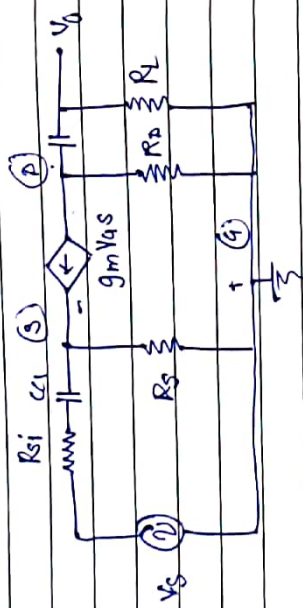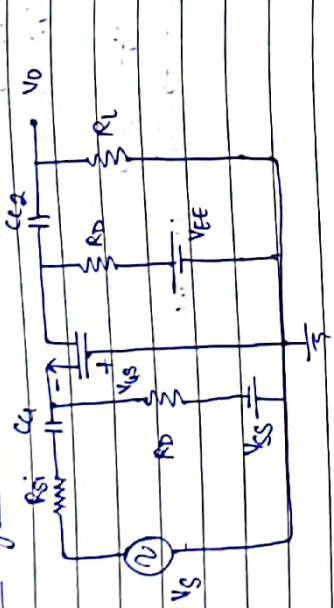

$$f_{LCL} = \frac{1}{2\pi [R_{Si} + (R_D \parallel r_o)] C_{C1}}$$

$$f_{HCL} = \frac{1}{2\pi [R_D + R_L] C_{C2}}$$

→ HF Analysis:

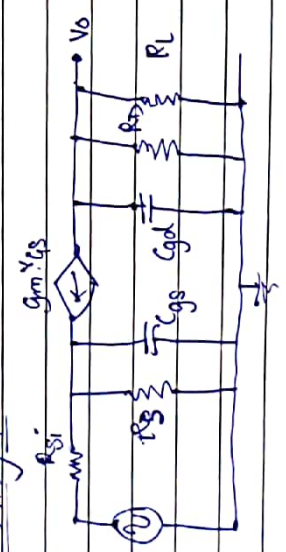


$$f_{HCL} = \frac{1}{2\pi [R_{Si} \parallel R_D \parallel \frac{1}{g_m}] C_{G1}}$$

$$f_{HCO} = \frac{1}{2\pi [R_D \parallel R_L] C_{C2}}$$


$$A_{V(mid)} = g_m (R_D \parallel R_L)$$

$$A_{V_S(mid)} = \frac{g_m (R_D \parallel R_L)}{1 + g_m R_{Si}}$$


* Common Drain MOSFET Amplifier:

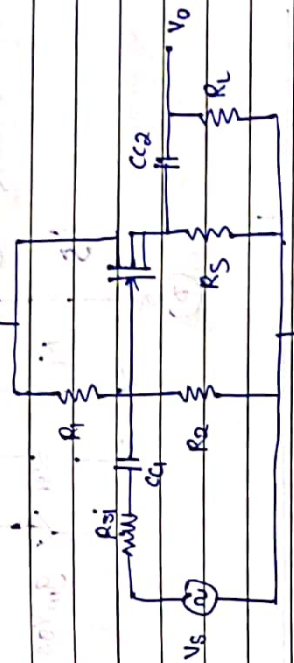

→ HF Analysis:

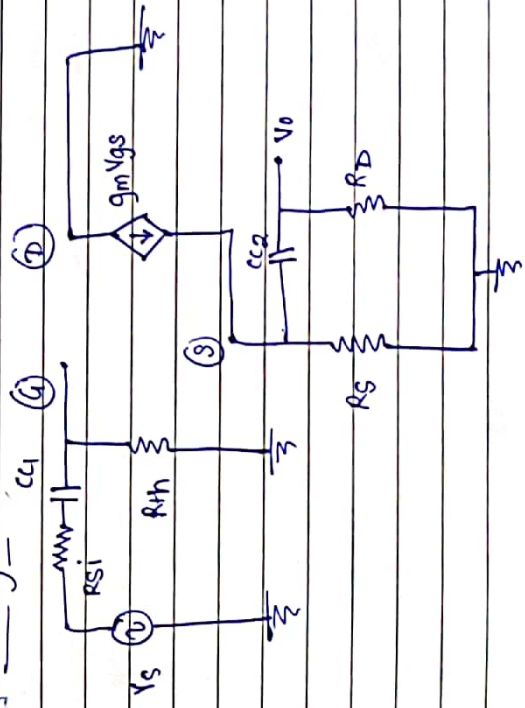


→ HF Analysis:

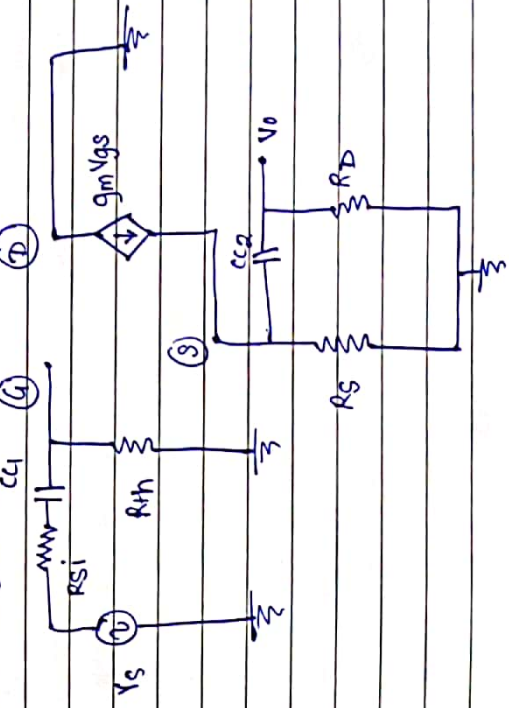

$$f_{mid} = \frac{1}{2\pi [R_S + R_{th}] C_u}$$

$$f_{upper} = \frac{1}{2\pi [R_L + (R_S \parallel R_{th})] C_u}$$

→ HF Analysis

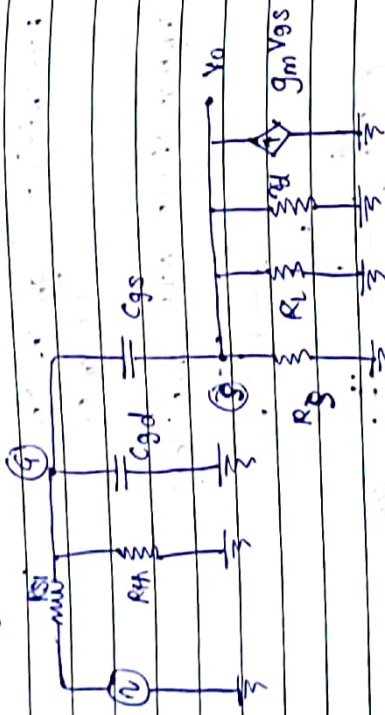

$$f_{HF} = \frac{1}{2\pi [R_S \parallel R_{th}] [C_{gd} + \frac{C_{gs}}{1 + g_m (R_S \parallel R_{th} \parallel R_L)}]}$$


• f_{mid}

* Short cut i gain of BJT transistor:

• $A_i = \frac{g_m r_{\pi}}{1 + g_m r_{\pi} (C_{\pi} C_u)} \rightarrow (HF \text{ SE } i \text{ gain})$

• $A_i = g_m r_{\pi} = \beta_0 \rightarrow (LF \text{ i gain})$

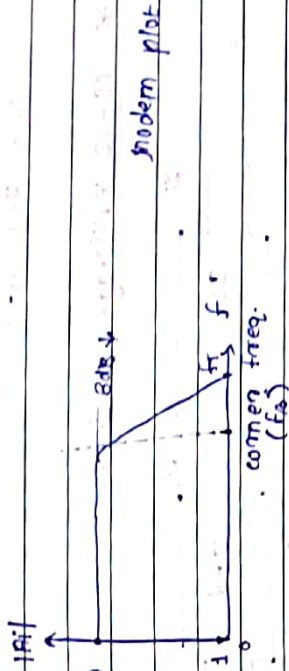• HF i gain is the funt of frequency whereas LF i gain is independent of freq.



$$f_{\beta} = \frac{1}{2\pi r_{\pi} (C_{\pi} + C_u)}$$

• Unity gain BW. (f_T) (ie. when $\beta_0 = 1$)

$$f_T = \beta_0 \cdot f_{\beta}$$

• gain ↓ BW ↓ $\rightarrow f_T$ (gain, BW product)

• gain ↑ BW ↓

q]

In certain BJT amp. $r_{\pi} = 2 \text{ k}\Omega$, $\beta = 100$ at 1 MHz , $\beta = 5$ at 20 MHz , determine the value of f_T , f_{β} and r_u . Assume: $C_u = 1 \text{ pF}$.

→ Soln.:

$$f_T = \beta \cdot f_{\beta}$$

→ when, $\beta = 100$

$$f_T = (100)(10^6) = 10^8 = 100 \text{ MHz}$$

→ when, $\beta = 5$

$$f_T = (5)(20)(10^6) = 100 \text{ MHz}$$

(BT)
 (MOSFET)
 $f_{in} = \frac{1}{2\pi \cdot g_m \cdot (C_g + C_d)}$
 $\therefore (10^6) = \frac{1}{2\pi \cdot (2 \times 10^{-3}) \cdot (C_g + 10^{-12})}$
 $C_g + 10^{-12} = \frac{1}{4\pi \cdot (10^6) \cdot (10^6)} = \frac{10^{-9}}{4\pi}$
 $C_g = 4.9 \cdot 10^{-12}$

* CS-CS Multistage Amplifier



$f_{LT} = \frac{f_{L1}}{\sqrt{2^n - 1}}$ n Stages
 $f_{HT} = f_{H1} \cdot (\sqrt{2^n - 1})$

a) Assume a 2 Stage amp, each stage has $f_L = 300$ Hz
 $f_H = 1000$ kHz, calculate BW of 2 Stage amp

$f_{LT} = \frac{(300)}{\sqrt{2^2 - 1}} = 466.25$ Hz
 $f_{HT} = (10^3) \cdot \sqrt{2^2 - 1} = 648.59$ kHz
 $\therefore BW = f_{HT} - f_{LT} = 648.96$ kHz
 $BW_{(single stage)} = 999.4$ kHz (calculated by taking $n=1$)
 In multistage amp, we get more gain, but compromising with BW

MS. amp :- 1) Cascade amp.
 types 2) cascode amp.

Advantages of Cascade amp


- Overall gain is improved;
- Impedance matching
 (in MS, loading effect of 1st g_m should not be on 2nd g_m
 i.e. $Z_{o1} \approx Z_{i2}$ (low $g_m \times$ of 1 & low $g_m \times$ of 2)
- types of coupling in MS. amp.
 • direct coupled (DC)
 • RC coupled
 • transformer coupled

RC coupled MS. amp is used, used to isolate the 2 stages using various techniques.

Disadvantage:

- compromization with BW.
- Ckt. is more complex, as Stages $\uparrow$, complexity $\uparrow$.

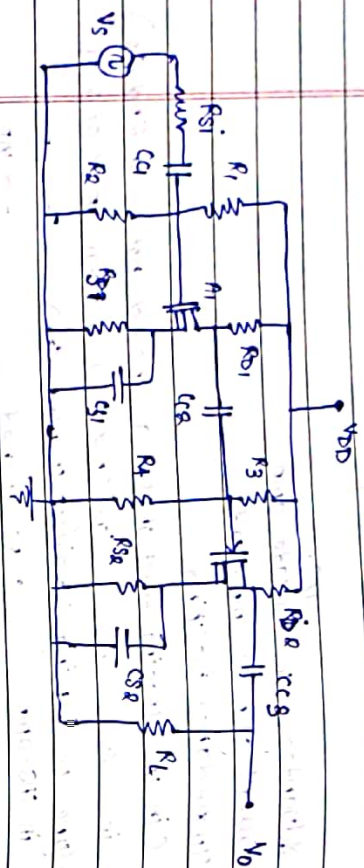* cascode cs-cs Multistage MOSFET Amplifier



a) Analysis: $\dots$ $Y_{it}(x)$

$$\frac{V_{th1}}{R_{th1}} = \frac{V_{DD} (R_2)}{R_1 + R_2}$$


$$V_{GS1} = V_G - I_{D1} R_{S1}$$

$$I_{D1} = k_{n1} \int v_{GS1} - v_{TN1} \int^{\infty}$$

$$V_{DS1} = V_{DD} - I_D (R_{D1} + R_{S1})$$

- $g_{HI} = 2K_{HI} [v_{is,1} - v_{tHI}]$

8] Mid freq. analysis:

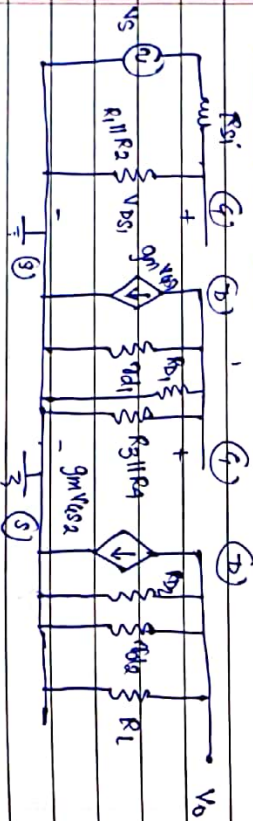

$$A_{y_1} = -g_{m_1} [r_{d_1} \parallel R_3 \parallel R_4] \parallel R_{o_1}$$

$$A_{y2} = -g_{m2} [r_{d2} \parallel R_L]$$


$$\therefore R_{r(mid)} = [R_{V1} \mid R_{V2}]$$

$$r_i = R_{si} + (R_{11}R_2)$$

$$Z_1 = Z_2 = \text{ad} \parallel R_3 \parallel R_4$$

$\gamma_{02} = \alpha_{02} \parallel R_L$

c) High Frequency Analysis:

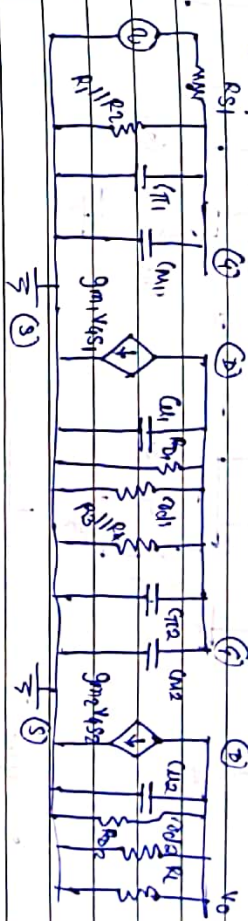

$$f_{\text{eff}} = \frac{1}{2\pi} \int_{R_{S1}}^{R_{S2}} \left(\frac{R_{S1}}{R} \right)^2 \left(\frac{R_{S2}}{R} \right)^2 \left(\frac{1}{C_{M1}} + \frac{1}{C_{M2}} \right) dR$$

here,

$$C_{M1} = C_{U1} \int (1 + \frac{1}{A_{U1}} \ln d) \frac{1}{d} dd$$


$$f_{H01} = f_{H12}$$

$$2\pi \left(\alpha_1 \parallel R_3 \parallel R_4 \right) \left(C_{U_1} + (C_{U_2} + C_{M_2}) \right) \parallel R_D$$

$$f_{\text{log}} = \frac{1}{\pi R_{\text{a}} \left(\sigma_{\text{a}} \parallel R_{\text{L}} \right) C_{\text{a}}}$$

lowest of 3 $\rightarrow$ 14

Low frequency analysis

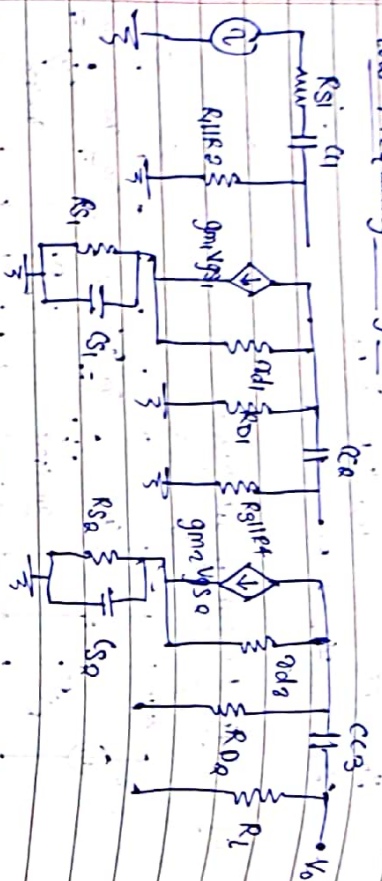

$$f_{ucl} = \frac{1}{2\pi [R_{S1} + R_{D1}R_2] C_1}$$


$$f_{ucl} = \frac{1}{2\pi [R_{D1} + R_{S1}R_2] C_2}$$

$$f_{ucl} = \frac{1}{2\pi [R_{D1} + R_L] C_3}$$

$$f_{ucl} = \frac{1}{2\pi [R_{S1} \parallel \frac{1}{g_{m1}}] C_1}$$

$$f_{ucl} = \frac{1}{2\pi [R_{S2} \parallel \frac{1}{g_{m2}}] C_2}$$

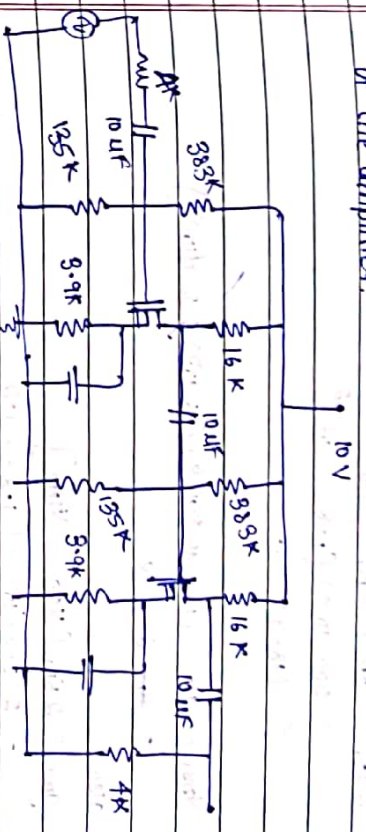Design for the given ckt CS-CS MOSFET amp. determine f_{mid} , $3dB$ f_L and BW of the amplifier.



$$K_{M1} = \frac{V_{DD}}{V_{GS1}} = 500 \mu A/V^2 \quad V_{TH1} = V_{TH2} = 1.2 V$$

$$K_{M2} = 200 \mu A/V^2$$

$$\lambda_1 = \lambda_2 = 0$$

$$V_{DD} = 10 V, \quad R_{S1} = R_{S2} = 3.9 K$$

$$R_1 = 383 K, \quad R_2 = 135 K$$

$$R_{D1} = 16 K = R_{D2}, \quad R_{S1} = 4 K$$

$$R_L = 4 K$$

$$C_1 = C_2 = C_3 = 10 \mu F$$

$$C_{gs} = 10 pF, \quad C_{gd} = 1 pF$$

$$C_{S1} = C_{S2} = 100 \mu F$$

Solution:

$$V_{TH1} = V_{TH2} = \frac{V_{DD} (R_2)}{R_1 + R_2}$$

$$= \frac{(10)(135)}{383 + 135} = 2.6 V$$

$$V_{GS1} = V_{GS2} = V_{TH1} - I_{D1} R_{S1}$$

$$= V_{TH1} - K_{M1} [V_{GS1} - V_{TH1}]^2 R_{S1}$$

$$= 2.6 - (500)(10^{-6}) [V_{GS1} - 1.2]^2 (3.9)(10^3)$$

$$\therefore V_{GS1} = 2.6 - 1950 (10^{-3}) [V_{GS1}^2 - 2.4 V_{GS1} + 1.44]$$

$$= 2.6 - 1.95 V_{GS1}^2 + 4.68 V_{GS1} - 2.8$$

$$\therefore -1.95 V_{GS1}^2 + 4.68 V_{GS1} - 0.2 = 0 \quad V_{GS1} = 1.83, \quad V_{GS2} = 0.056$$

Now, $V_{GS} > V_{TH1}$

$$\begin{aligned} \therefore V_{GS} &= 1.83 \text{ V} \\ \therefore I_{D1} &= K_{N1} [V_{GS} - V_{TH1}]^2 \\ &= 500 (10^{-6}) [1.83 - 1.2]^2 \\ &= 198.45 \text{ } \mu\text{A} \end{aligned}$$

$$\begin{aligned} V_{DS1} &= 10 - (198.45)(10^{-6})(16(10^3) + 3.9(10^3)) \\ &= 6.05 \text{ V} \end{aligned}$$

also

$$\begin{aligned} g_{m1} &= 2K_{N1} [V_{GS} - V_{TH1}] \\ &= 2(500)(10^{-6}) [1.83 - 1.2] \\ &= 0.63 \text{ mS} \end{aligned}$$

→ AC Analysis

For CS (II) $\rightarrow V_{TH2} = V_{GS} = \frac{(10)(135)(10^3)}{1 + 518(10^3)}$

$$\therefore V_{TH2} = 2.6 \text{ V}$$

$$\begin{aligned} V_{GS2} &= V_{GS} - I_{D2} R_{S2} \\ &= 2.6 - (200)(10^{-3}) [V_{GS2} - 1.2]^2 (3.9) \\ &= 2.6 - 0.78 [V_{GS2}^2 - 2.4 V_{GS2} + 1.44] \\ &= 2.6 - 0.78 V_{GS2}^2 + 1.872 V_{GS2} - 1.1232 \\ \therefore -0.78 V_{GS2}^2 + 1.872 V_{GS2} + 1.48 &= 0 \\ \therefore V_{GS2} &= 2.044 \text{ V} \end{aligned}$$


$$\begin{aligned} \therefore I_{D2} &= K_{N2} [V_{GS2} - V_{TH2}]^2 \\ &= (200)(10^{-6}) [2.044 - 1.2]^2 \\ &= 142.4 \text{ } \mu\text{A} \end{aligned}$$

$$\begin{aligned} V_{DS2} &= 10 - (142.4)(10^{-3})(19.9) \\ &= 7.166 \text{ V} \end{aligned}$$

$$\therefore g_{m2} = 0.332 \text{ mS}$$

$$A_{V1} =$$

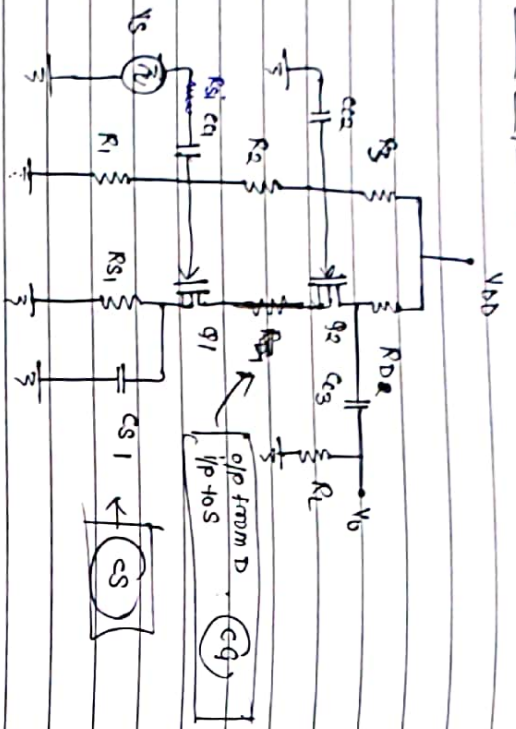* Common Source Amplifier: CS-CM MOSFET Amplifier



- Good gain and Good BW.

→ DC Analysis:

i). $V_{GS1} = V_{G1} - I_{D1} R_S$

$V_{G1} = \frac{V_{DD} \cdot R_1}{R_1 + R_2 + R_3}$

• $I_{D1} = K_{N1} [V_{GS1} - V_{TN}]^2$ $V_{S1} = I_{D1} \cdot R_S$

$V_{GS1} = V_{D1}$

ii). $V_{GS2} = V_{G2} - V_{S2}$

here,

$V_{G2} = \frac{V_{DD} (R_1 + R_2)}{R_1 + R_2 + R_3}$

here, $V_{S2} = V_{D1} - V_{S1}$

$V_{D2} = V_{DD} - I_{D2} R_{D2} R_D$

$V_{S2} = V_{D2} - V_{S2}$

$= V_{D2} - V_{D1} \quad (\text{here } V_{S2} = V_{D1})$

g)

$V_{GS2} = V_{G2} - V_{S2}$

∴ Both transistors are identical will be given in question

$V_{DD} = 10 \text{ V}, R_3 = 95 \text{ k}\Omega, R_2 = 150 \text{ k}\Omega, R_1 = 55 \text{ k}\Omega$

$R_S = 10 \text{ k}\Omega, R_D = 2.5 \text{ k}\Omega, K_{N1} = 2 \text{ mA/V}^2, K_{N2} = 1 \text{ mA/V}^2$

$V_{TN1} = V_{TN2} = 0.5 \text{ V}$

$C_{C1} = C_{C2} = C_{C3} = 10 \text{ }\mu\text{F}, C_S = 100 \text{ }\mu\text{F}$

→ Solution:

i). $V_{G1} = \frac{V_{DD} R_1}{R_1 + R_2 + R_3} = \frac{(10)(55)(10^3)}{250 \text{ } 300 \text{ k}\Omega} = 1.83 \text{ V}$

$V_{GS1} = V_{G1} - I_{D1} R_S$

$= V_{G1} - K_{N1} [V_{GS1} - V_{TN}]^2 R_S$

$= 1.83 - (2)(10^{-3}) [V_{GS1} - 0.5]^2 10(10^3)$

$= 1.83 - 20 [V_{GS1}^2 - V_{GS1} + 0.25]$

$= 1.83 - [20 V_{GS1}^2 - 20 V_{GS1} + 5]$

∴ $V_{GS1} = 1.83 - 20 V_{GS1}^2 + 20 V_{GS1} - 5$

∴ $20 V_{GS1}^2 - 19 V_{GS1} + 3.17 = 0$

∴ $V_{GS1} = 0.73 \text{ V}, 0.21$

$I_{D1} = K_{N1} [V_{GS1} - V_{TN}]^2$ $V_{S1} = (105.8)(10^{-6})$

$= (2)(10^{-3}) [0.73 - 0.5]^2$ $= 1.058 \text{ V}$


$= 0.1058 \text{ mA}$

ii). $V_{G2} = \frac{V_{DD} (R_1 + R_2)}{R_1 + R_2 + R_3} = \frac{(10)(205)(10^3)}{300(10^3)}$

$= 6.83 \text{ V}$

Mid frequency analysis:

• Drawing small signal model

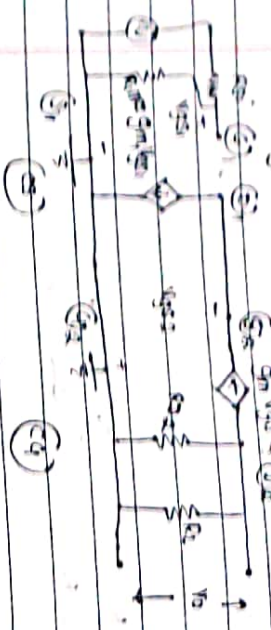

$$Z_i = R_{S1} \parallel R_L$$

$$A_{vi} = \frac{v_o}{v_i} = \frac{-g_{m1} v_{gs1} (R_{D1} \parallel R_L)}{v_{gs1}} = -1$$

$$A_{v2} = \frac{v_o}{v_i} = \frac{-g_{m2} v_{gs2} (R_{D2} \parallel R_L)}{-v_{gs2}} = g_{m2} (R_{D2} \parallel R_L)$$

• N/A

$$A_{v1} = A_{v1} \cdot A_{v2}$$

$$A_{v1} = -g_{m1} (R_{S1} \parallel R_L)$$


∴ both transistors are identical

$$g_{m1} = g_{m2}$$

$$A_{v1} = -g_{m1} (R_{S1} \parallel R_L)$$

• The total A_v of cascade amplifier is same as single stage amplifier

High frequency analysis:


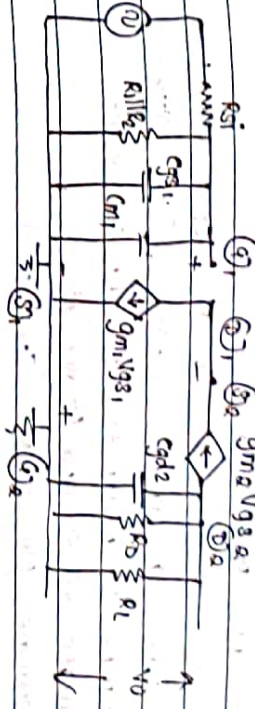


$$F_{H1} = \frac{1}{2\pi (R_{S1} \parallel R_L \parallel R_{D1}) (C_{gs1} + C_{m1})}$$

$$C_{m1} = C_{gd1} [1 + g_{m1} v_{gs1} (R_{D1} \parallel R_L)]$$

$$F_{H0} = \frac{1}{2\pi (R_{D2} \parallel R_L) C_{gd2}}$$

Low frequency analysis:

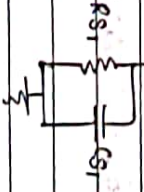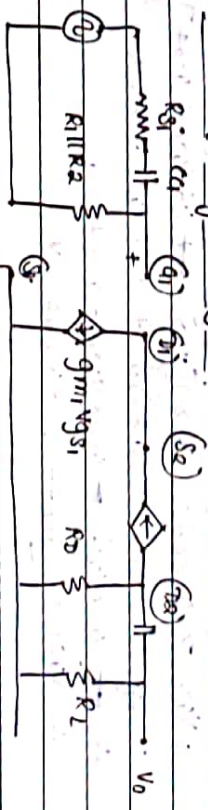

$$f_{L1} = \frac{1}{2\pi (R_{S1} + R_{L1}) C_{S1}}$$

$$f_{L2} = \frac{1}{2\pi (R_{D1} + R_L) C_{D1}}$$

$$f_{L3} = \frac{1}{2\pi (R_{S1} \parallel \frac{1}{g_{m1}}) C_{S1}}$$

q) For the ckt dgm: $R_1 = 12k\Omega$, $R_2 = 24k\Omega$, $R_3 = 100k\Omega$, $R_S = 1k\Omega$, $R_D = 3.3k\Omega$, $C_{C1} = C_{C2} = 10\mu F$, $C_S = 100\mu F$, $V_{DD} = 10V$, $R_{S1} = 1k\Omega$, $R_L = 10k\Omega$, $[K_{N1} = K_{N2} = 0.8mA/V^2]$, $[V_{TN1} = V_{TN2} = 0.8V]$
Determine DC parameters of given cascade ckt,
Calculate Z_i , Z_o and A_v for ckt.
Determine BW of ckt. ($I_{D1} = I_{D2}$)

→ Solution:

a) DC Analysis:

$$V_{G1} = \frac{V_{DD} \cdot R_1}{R_1 + R_2 + R_3} = \frac{(10)(12)(10^3)}{136(10^3)} = 0.882V$$

$$\begin{aligned} \text{Now, } V_{GS1} &= V_{G1} - I_{D1} R_S \\ &= 0.882 - (0.8)(10^{-3})[V_{GS1} - 0.8]^2 (1)(10^3) \\ \therefore V_{GS1} &= 0.882 - (0.8)[V_{GS1}^2 - 1.6V_{GS1} + 0.64] \\ \therefore V_{GS1} &= 0.882 - 0.8V_{GS1}^2 + 1.28V_{GS1} - 0.512 \\ \therefore 0.8V_{GS1}^2 - 0.28V_{GS1} - 0.34 &= 0 \\ \therefore V_{GS1} &= 0.877, -0.527V \end{aligned}$$

$$\begin{aligned} I_{D1} &= (0.8)(10^{-3})(0.877 - 0.8)^2 (10^3) \\ \therefore I_{D1} &= 4.74\mu A \end{aligned}$$

$$V_{G2} = \frac{V_{DD} (R_1 + R_2)}{136(10^3)} = \frac{36(10^3)}{136(10^3)} = 2.647V$$

$$\begin{aligned} \text{Now, } V_{GS2} &= V_{G2} - I_{D2} (R_{S2}) \\ &= 2.647 - (4.74)(10^{-6})(1) \\ &= 2.63 \end{aligned}$$

$$\begin{aligned} \rightarrow V_{DS} &= V_{DD} - I_{D2} R_D \\ &= 10 - (4.74)(10^{-6})(3.3)(10^3) \\ &= 9.99V \end{aligned}$$

$$\begin{aligned} V_{GS1} &= I_{D1} R_{S1} \\ &= (4.74)(10^{-6})(1)(10^3) \\ &= 4.74mV \end{aligned}$$

$$\begin{aligned} \text{Now, } V_{GS2} &= V_{D1} \\ \text{Now, } V_{DS2} &= V \end{aligned}$$

$$\begin{aligned} \rightarrow \text{Thus, } \therefore I_{D1} &= I_{D2} \text{ and } V_{TN1} = V_{TN2} \text{ \& } K_{N1} = K_{N2} \\ \therefore V_{GS1} &= V_{GS2} = 0.877V \end{aligned}$$


$$\begin{aligned} \text{b) Now, } g_m &= 2K_N (V_{GS} - V_{TN}) \\ &= 2(0.8)(10^{-3})(0.877 - 0.8) \\ &= 0.1232mS \end{aligned}$$

$$\begin{aligned} \therefore |A_{vmid}| &= 0.1232(10^{-3})(3.3k || 10k) \\ &= 0.305 \end{aligned}$$

$$\text{c) } f_{cut} = \frac{1}{2\pi(R_{S1} + R_{in} || R_D)C_{C1}}$$

* Darlington Amplifier: (cc-cc pair)

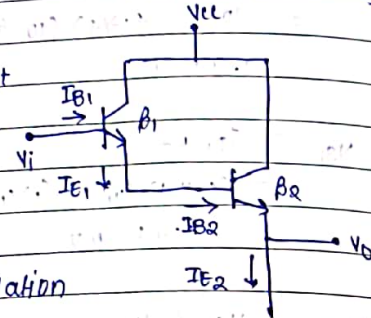- used to improve current gain in amplifier. It has high i/p $\times$ and low o/p $\times$
- It can be used as a buffer amplifier for isolation purpose
- Not used for v-amplification, coz A_v for cc is always 1




$$A_i = \frac{I_{E2}}{I_{B1}} = \frac{(1+\beta_2) I_{B2}}{I_{B1}}$$


But, $I_{B2} = I_{E1} = (1+\beta_1) I_{B1}$

$$\therefore A_i = \frac{(1+\beta_2)(1+\beta_1) I_{B1}}{I_{B1}}$$
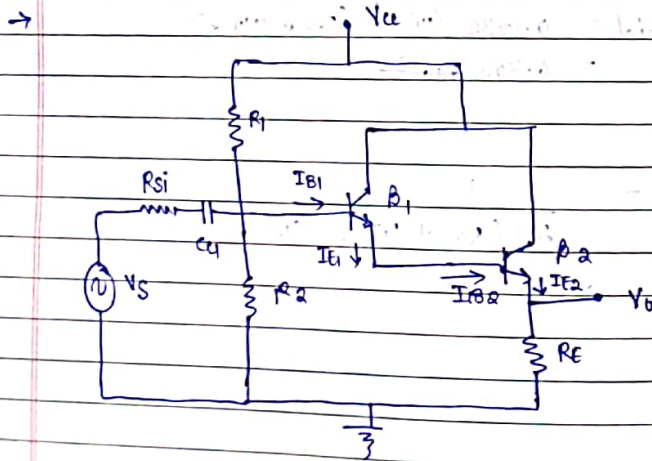
$$\therefore A_i = (1+\beta_2)(1+\beta_1) \approx \beta_1 \beta_2 \approx \beta^2$$



→ DC equivalent ckt:

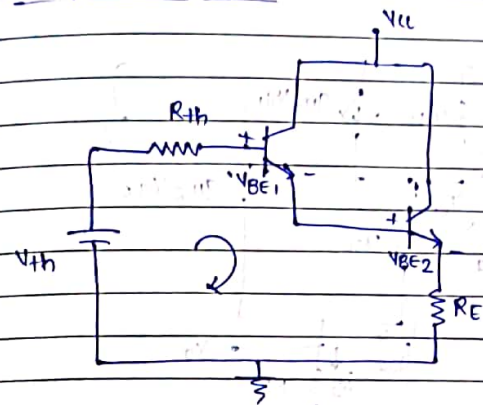

$$V_{Th} = \frac{V_{CC} \cdot R_2}{R_1 + R_2}, \quad R_{Th} = R_1 \parallel R_2$$

Now,

$$V_{Th} - I_{B1} R_{Th} - V_{BE1} - V_{BE2} - I_{E2} R_E = 0$$

$$\therefore I_{B1} = \frac{V_{Th} - V_{BE1} - V_{BE2}}{R_{Th} + \beta_D R_E}$$

here,

$$I_{E2} = (1+\beta_2) I_{B2}$$

$$= (1+\beta_2)(1+\beta_1) I_{B1} \approx \beta_1 \beta_2 I_{B1}$$

$$\therefore I_{E2} \approx \beta_D \cdot I_{B1}$$

$$I_{C1} = \beta_1 I_{B1}$$

$$\text{Now, } V_{CC} - V_{CE2} - I_{E2} R_E = 0$$


$$\therefore V_{CE2} = V_{CC} - I_{E2} R_E$$

$$I_{E1} = I_{C1} + I_{B1}$$

$$I_{C2} = \beta_2 I_{B2}$$

$$V_{E2} = I_{E2} R_E$$

→ Hybrid- π model

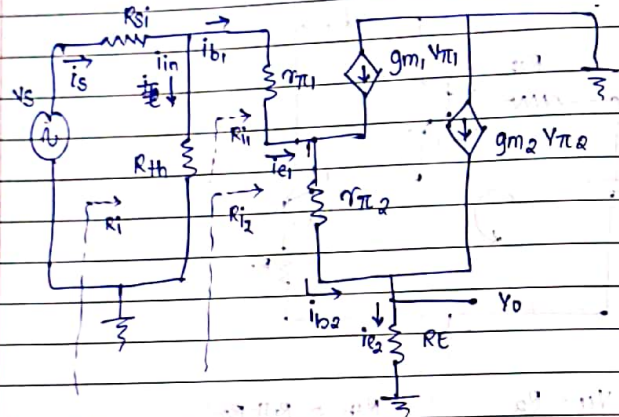

→ Total i/p R :

- $R_{in} = R_{si} + R_i$
- Now, $R_i = R_{th} \parallel R_{i1}$
- here, $R_{i1} = r_{\pi 1} + (1 + \beta_1) [r_{\pi 2} + (1 + \beta_2) R_E]$

Thus,

$$\Rightarrow R_{in} = R_{si} + \left[R_{th} \parallel \left(r_{\pi 1} + (1 + \beta_1) [r_{\pi 2} + (1 + \beta_2) R_E] \right) \right]$$

→ O/p R :

- $R_o = R_E \parallel R_{o1}$

$$\text{Now, } R_{o1} = \frac{R_{o2} + r_{\pi 2}}{1 + \beta_2}$$

$$\text{here, } R_{o2} = \frac{R_{si} \parallel R_{th} \parallel R_{i1}}{1 + \beta_1}$$

$$\Rightarrow R_o = R_E \parallel \left[\frac{\left(\frac{R_{si} \parallel R_{th} \parallel R_{i1}}{1 + \beta_1} \right) + r_{\pi 2}}{1 + \beta_2} \right]$$

→ Current gain:

$$A_i = \frac{i_{e2}}{i_s}$$

$$\text{Now, } A_i = \frac{i_{e2}}{i_{b2}} \cdot \frac{i_{b2}}{i_{e1}} \cdot \frac{i_{e1}}{i_{b1}} \cdot \frac{i_{b1}}{i_{in}} \cdot \frac{i_{in}}{i_s}$$

$$= (1 + \beta_2) (1) (1 + \beta_1) \left[\frac{R_{th}}{R_{th} + R_{i1}} \right] \left[\frac{R_{si}}{R_{si} + R_i} \right]$$


$$\Rightarrow A_i = \beta_D \left[\frac{R_{th}}{R_{th} + R_{i1}} \right] \left[\frac{R_{si}}{R_{si} + R_i} \right]$$

* const. current source biasing:(A) 2 transistor const. current source
(Current Mirror):

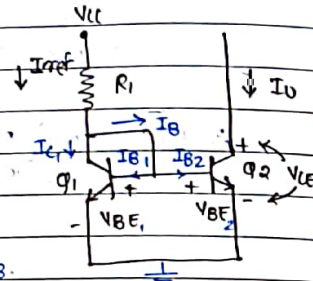- E. of both Qs are tied together and collector of both Qs connected to base.

$\therefore Q_1$ will act as a diode

- As V_{CC} is applied to Q_1 , I_{ref} will flow making Q_1 - FB. and as Q_1 gets FB, Q_2 will also get FB. and I_o flows through Q_2 line



- KVL on i/p side

$$\therefore V_{CC} - I_{ref} \cdot R_1 - V_{BE1} = 0$$

$$\therefore I_{ref} = \frac{V_{CC} - V_{BE1}}{R_1}$$

$$\text{Also, } I_{ref} = I_{C1} + I_B = I_{C1} + I_{B1} + I_{B2}$$

$\therefore$ Bases are tied together $\Rightarrow I_{B1} = I_{B2}$


$$\therefore I_{ref} = I_{C1} + 2I_{B2} = I_{C1} + \frac{2I_{C2}}{\beta}$$

$\therefore Q_1$ & Q_2 are identical $\therefore I_{C1} = I_{C2}$

$$\therefore I_{ref} = I_{C2} + \frac{2I_{C2}}{\beta}$$

$$= I_{C2} \left[1 + \frac{2}{\beta} \right]$$
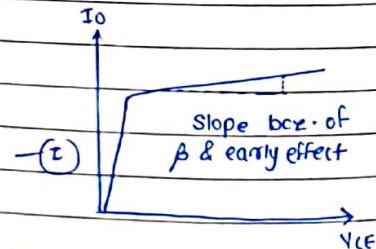
$$\therefore I_{C2} = I_o = \frac{I_{ref}}{\left[1 + \frac{2}{\beta} \right]} \quad \text{--- (I)}$$



$$\therefore \frac{I_o}{I_{ref}} = \frac{1}{\left[1 + \frac{2}{\beta} \right]} \cdot \frac{\left(1 + \frac{V_{CE2}}{V_A} \right)}{\left(1 + \frac{V_{CE1}}{V_A} \right)} \quad \text{here } V_A: \text{early v.}$$

- Now, from adj. dgm.

$$\rightarrow V_{CE2} = V_i - V_{BE} \quad \text{--- (II)}$$

$$\rightarrow V_{CE1} = V_{BE} \quad \text{--- (III)}$$

Now,



$$\frac{dI_o}{dV_{CE2}} = \frac{I_{ref}}{\left[1 + \frac{2}{\beta} \right]} \cdot \frac{\left(\frac{1}{V_A} \right)}{\left(1 + \frac{V_{BE}}{V_A} \right)}$$

$$\therefore \frac{1}{r_o} = \frac{I_{ref}}{\left[1 + \frac{2}{\beta} \right]} \cdot \frac{1}{V_A} \rightarrow \text{from (I)(II)(III)}$$

$$\therefore \frac{1}{r_o} = \frac{I_o}{V_A} \quad \therefore r_o = \frac{V_A}{I_o}$$

$\rightarrow r_o \propto \infty$ to achieve const. current source

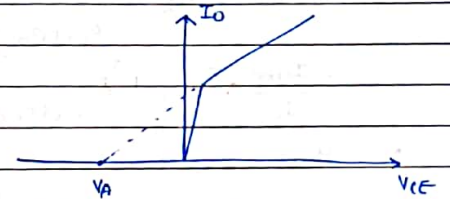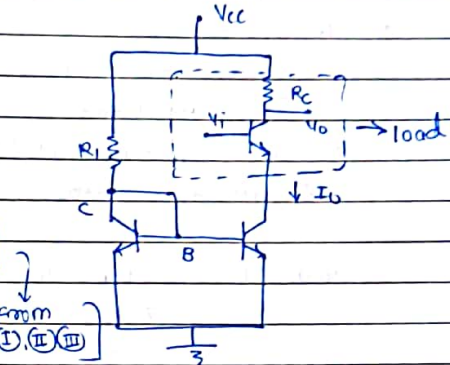$\rightarrow$ Independent of β $\rightarrow$ condns. to get good const. current source



q] Describe 2 q - const. i source & derive relationship betn. I_o & I_{ref}

q] Explain the effect of r_o in const. i source

(B) Basic 3 transistor current source:


- Q_3 supplies base current I_{B1} & I_{B2} to Q_1 & Q_2 resp.

- Here, $I_{B1} = I_{B2}$
 $I_{C1} = I_{C2}$ ($\because Q_1, Q_2$ identical)

$$I_{ref} = I_{C1} + I_{B3}$$

$$\rightarrow I_{E3} = I_{B1} + I_{B2} \quad (\text{KCL at } Q_3)$$

$$\therefore (1+\beta)I_{B3} = 2I_{B2}$$

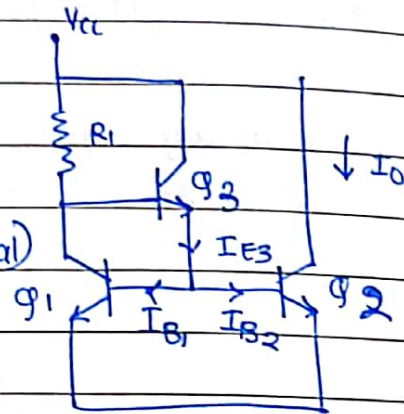

$$\text{Now, } I_{ref} = I_{C1} + I_{B3}$$

$$= I_{C1} + \frac{I_{E3}}{1+\beta_3} = I_{C1} + \frac{2I_{B2}}{1+\beta_3}$$

$$\therefore I_{ref} = I_{C2} + \frac{2I_{C2}}{\beta(1+\beta_3)}$$

$$\therefore \frac{I_{ref}}{I_{C2}} = \left[1 + \frac{2}{\beta(1+\beta_3)} \right]$$

- thus, $I_{C2} = I_O = \frac{I_{ref}}{\left[1 + \frac{2}{\beta(1+\beta_3)} \right]}$

$\rightarrow$ here, in improved version of 3-g^{current} source, change in load current with change in β is much smaller than 2-g current source

- $I_{ref} = \frac{V_{CC} - V_{BE3} - V_{BE}}{R_1}$