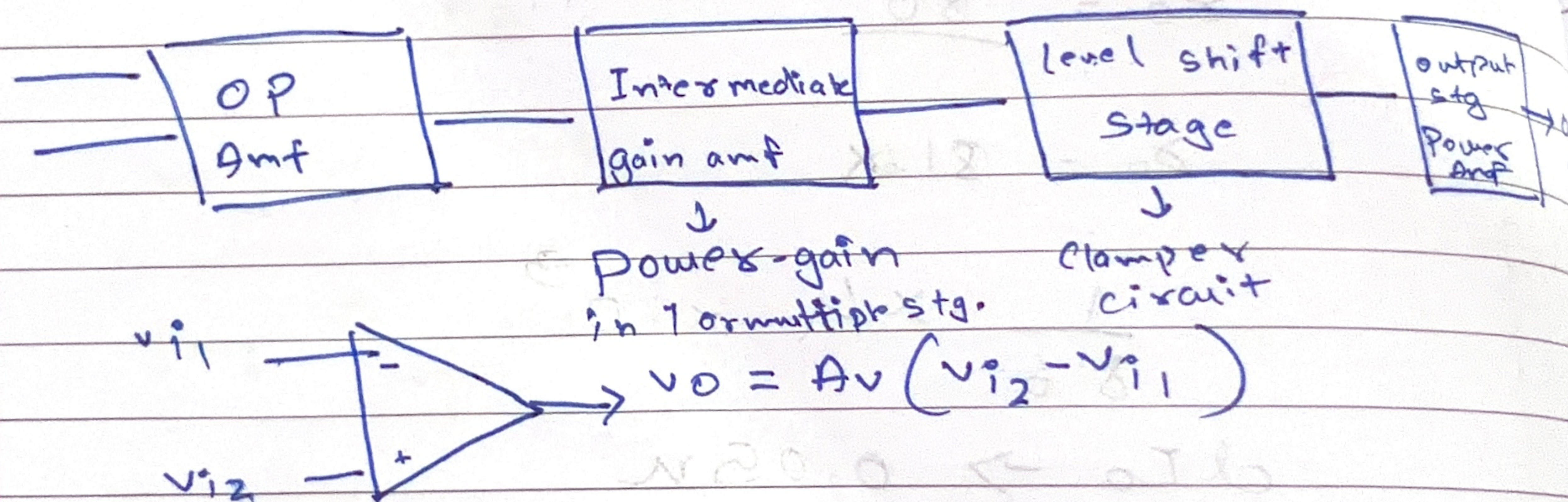


Module - 3

Op-amp $\rightarrow$ is a high gain, high input impedance and no O/P impedance and integrated circuit DC amp. It comprises of 4 stages

- i) Diff amp
- ii) gain
- iii) level shifter stage
- iv) output power amp.




Features of Op Amp

- i) Inf. differential voltage gain $A_{od} = \frac{V_o}{V_i} = \frac{V_o}{v_{i2} - v_{i1}} = \infty$
- ii) Inf. i/p impedance, $I_1 = I_2 = 0$, $R_{in} = \infty$
- iii) 0 o/p impedance, O/P is directly taken from the load it is independent of the load.
- iv) 0 o/p voltage, when I/P v is Zero
- v) Inf CMRR (common mode rejection ratio).

ii) Inf. slew rate

iii) 0 SVRR

Op amp works in open loop

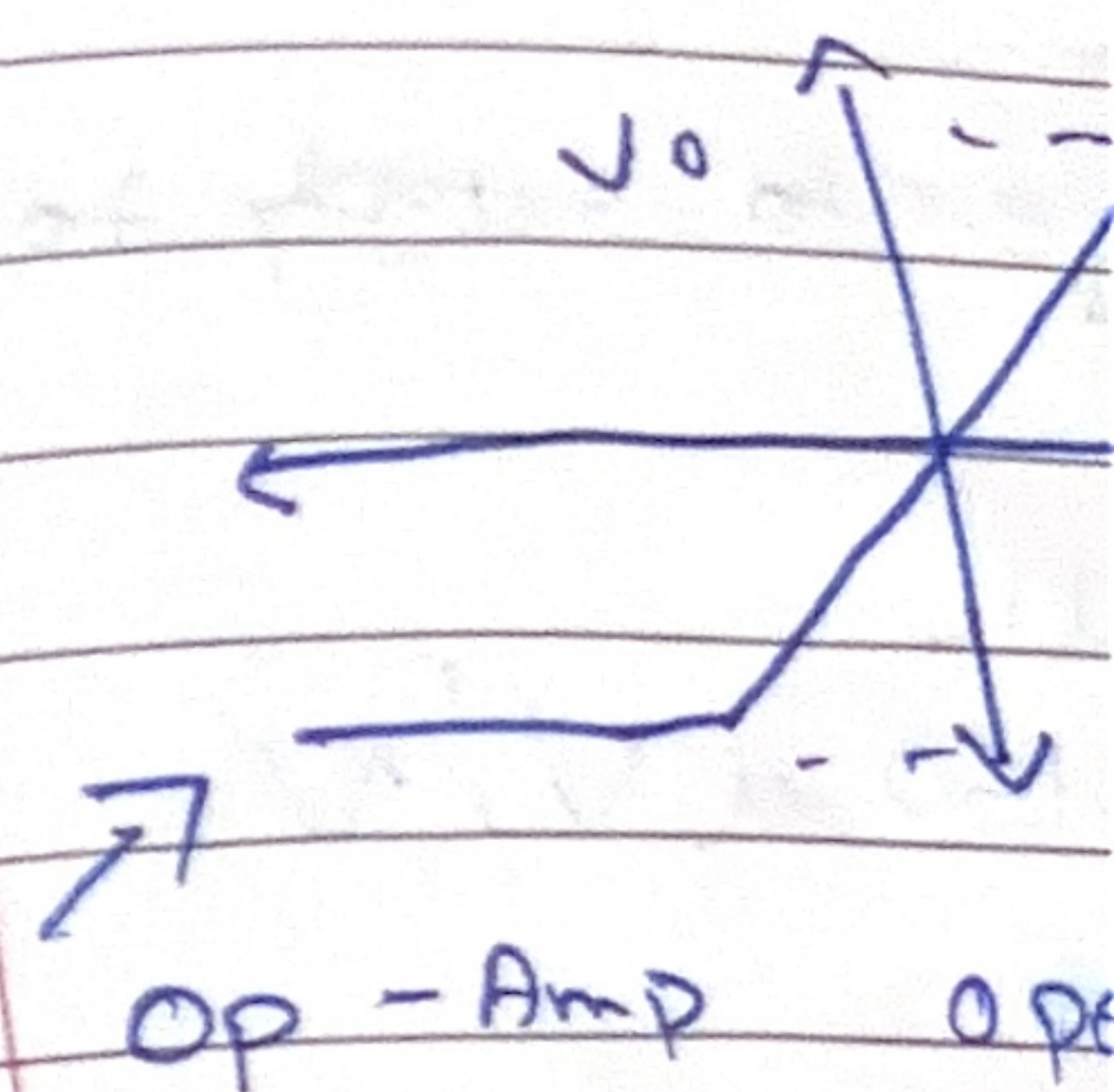

Practical

i) O/P of voltage I/P signal mV.

ii) I/P def btw to

iii) I/P I:

iv) I/


v) 0

vi) Inf. slew rate

vii) 0 SVRR (Supplied Voltage rejection ratio).

Op amp works in 2 way

open loop closed loop.

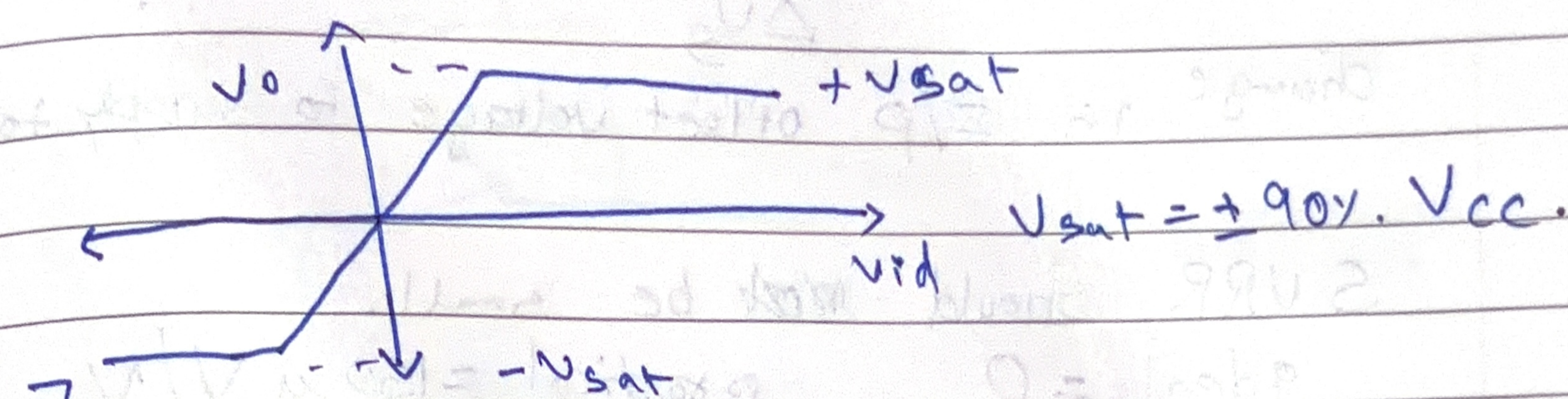

Op-Amp open loop, rarely used bec of saturation

Practical features of Op-Amp

i) O/p offset voltage

voltage obtained at the o/p terminals without any I/P signal applied. denoted by (V_{oo}) ideally in mV.

ii) I/P offset voltage

def as the amount of voltage to be applied btwn 2 I/P terminals such that the V_{oo} reduces to zero (0). $\rightarrow$ denoted by (V_{IO}).

iii) I/P offset current

$$I_{io} = |I_2 - I_1| \approx \text{nano ampere}$$

iv) I/P bias current $\rightarrow I_B = \frac{I_1 + I_2}{2}$

v) CMRR, it is the ratio of differential gain to common mode gain.

$$A_d/A_c \rightarrow A_d = V_o/v_{id} \quad A_c = V_o/v_i$$

ideally $A_d \rightarrow \infty$ $A_c \rightarrow 0$ $CMRR \rightarrow \infty$

Practical $CMRR \approx 90dB$

vi) large signal voltage gain, $A_d = \frac{V_o}{V_{id}}$

vii) $SURR = \frac{\Delta V_{io}}{\Delta V_s}$ it is the ratio of
change in I/P offset voltage to supply to O/P.

$SURR$ should not be small.

ideal = 0 practical = $150 \mu V/V$


viii) Slew rate $\rightarrow$ maximum rate of change of
O/P voltage per time.

$\left. \frac{dV_o}{dt} \right|_{\max} \approx 0.5 V/\mu sec$
(practical)

Speed of Op-Amp

ix) I/P impedance $\approx 1 M\Omega$ [practical]
O/P $\approx 100 \Omega$

frequency response of ~~Op-amp~~ op-amp.

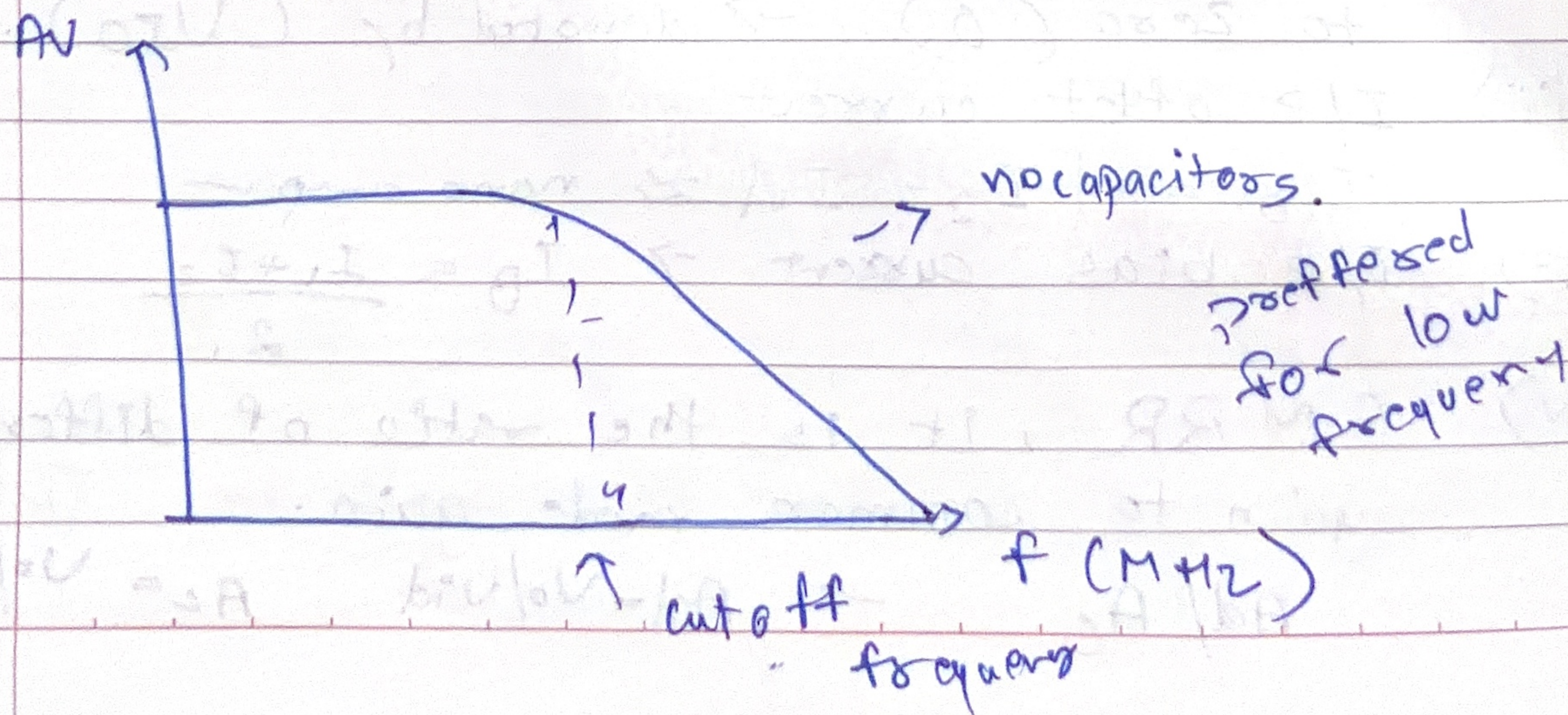




Also called as D

Closed loop

i) inverting amp

ii) non-inverting amp

iii) differential

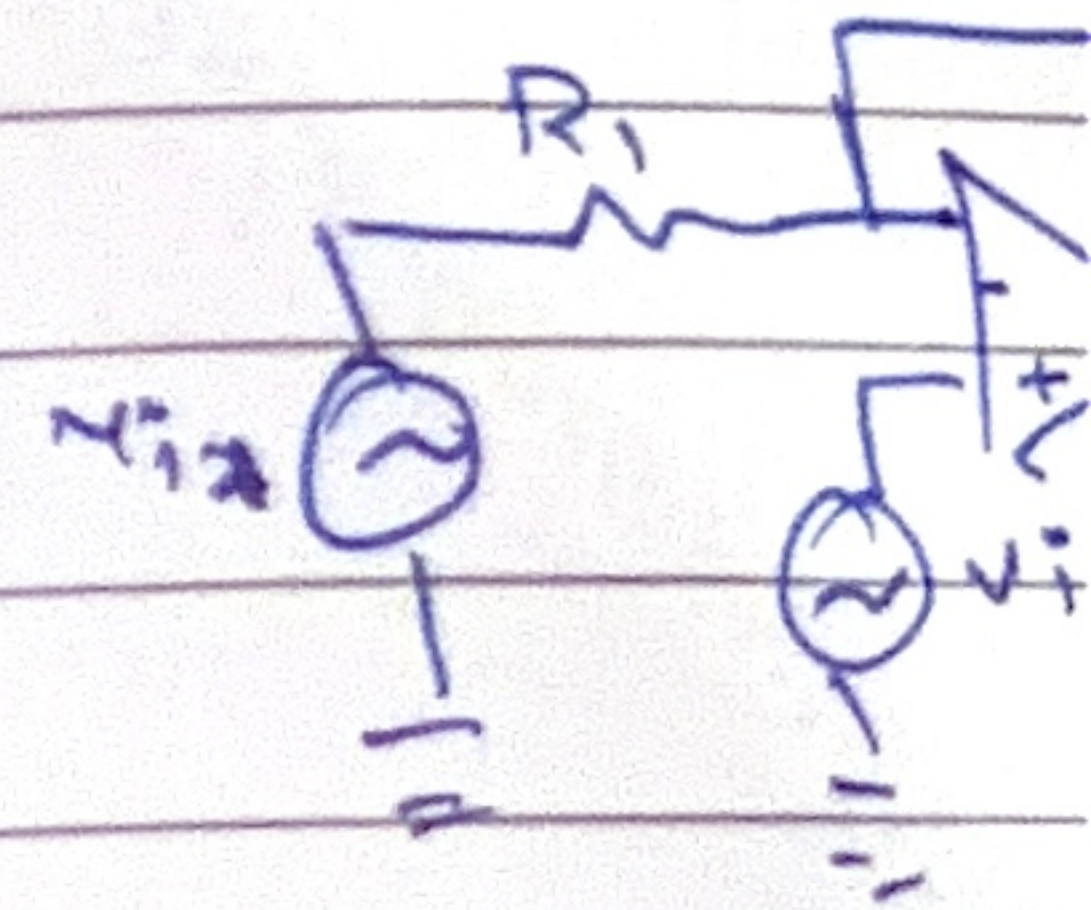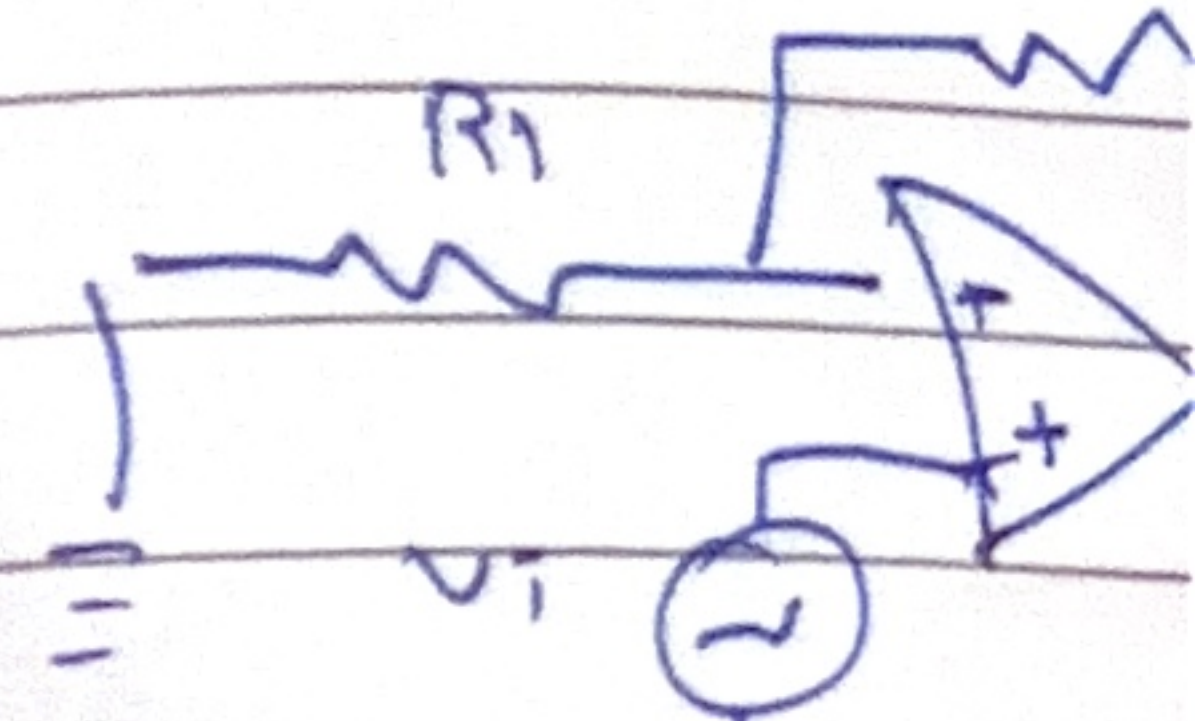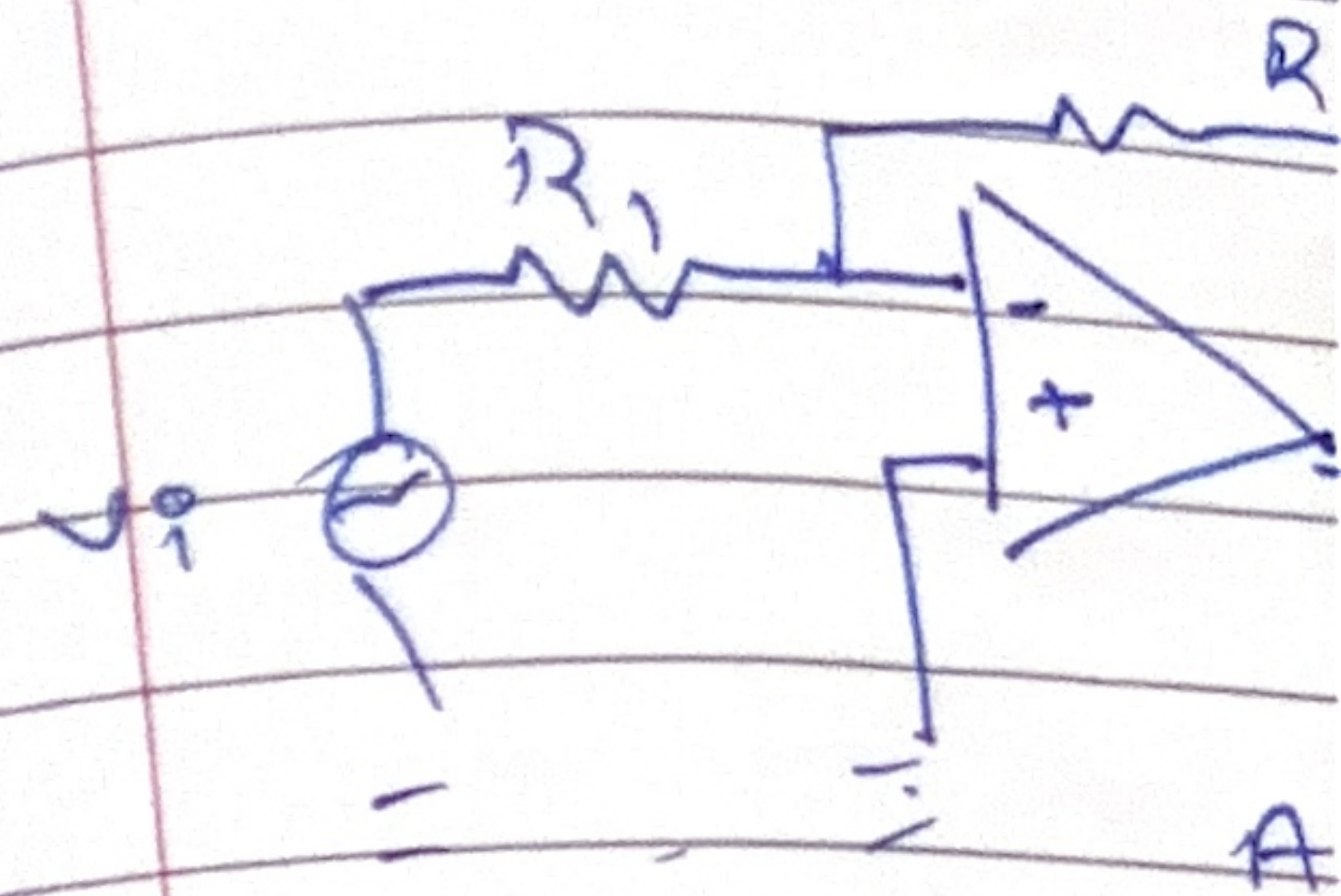

MRR $\rightarrow \infty$

$\frac{V_o}{V_{id}}$
ratio of

supply to o/p.

V/V

range of

)

[Practical]

op-amp.

used
low
frequency

Also called as DC ampf.

Closed loop Op-Amp

- i) Inverting ampf.
- ii) non-inverting ampf
- iii) differential ampf.

