



TITLE: Performance evaluation of different types of Constant Current Source

AIM: To evaluate the output resistance of different types of constant current source using LtSpice.


OUTCOME: Students will be able to understand the basics of analog Integrated Circuits

PROCEDURE:

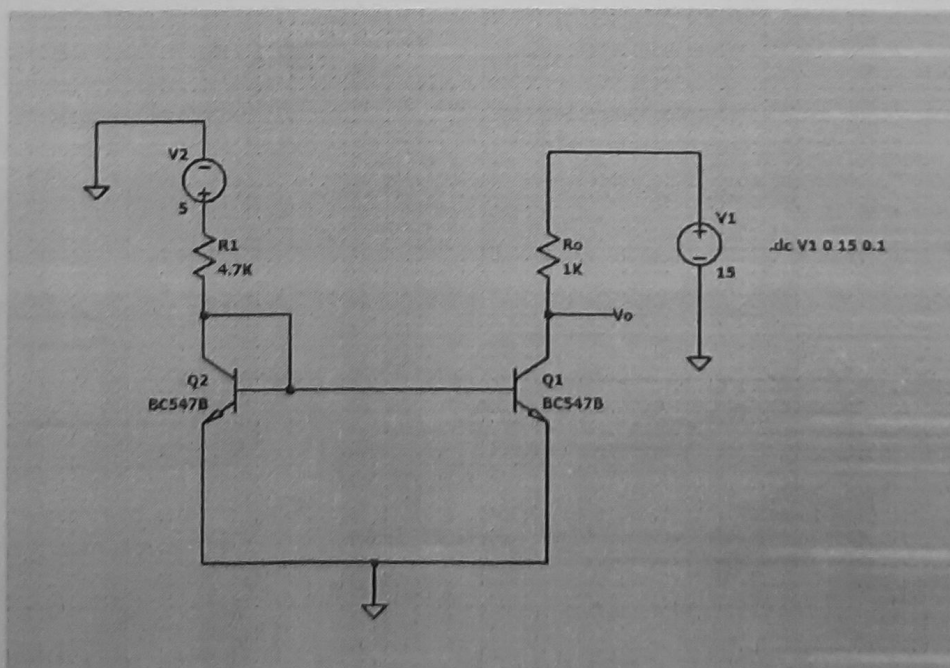
1. Implement the basic two transistor constant current biasing circuit using LtSpice.
2. Adjust V_{cc} such that $I_{ref} = 1 \text{ mA}$.
3. Find the values of I_o and V_{CE} (collector voltage) as V_s is varied from 15V to 0V as per the observation table I.
4. Find the dynamic output resistance by plotting I_o versus V_{CE} curve.
5. Repeat above procedure in workspace of Ltspice for Wilson and Widlar constant current biasing circuit.
6. Comment on the output resistance offered by each circuit.

Circuit Diagram


Basic Two Transistor Constant Current Source




Wilson Constant Current Source

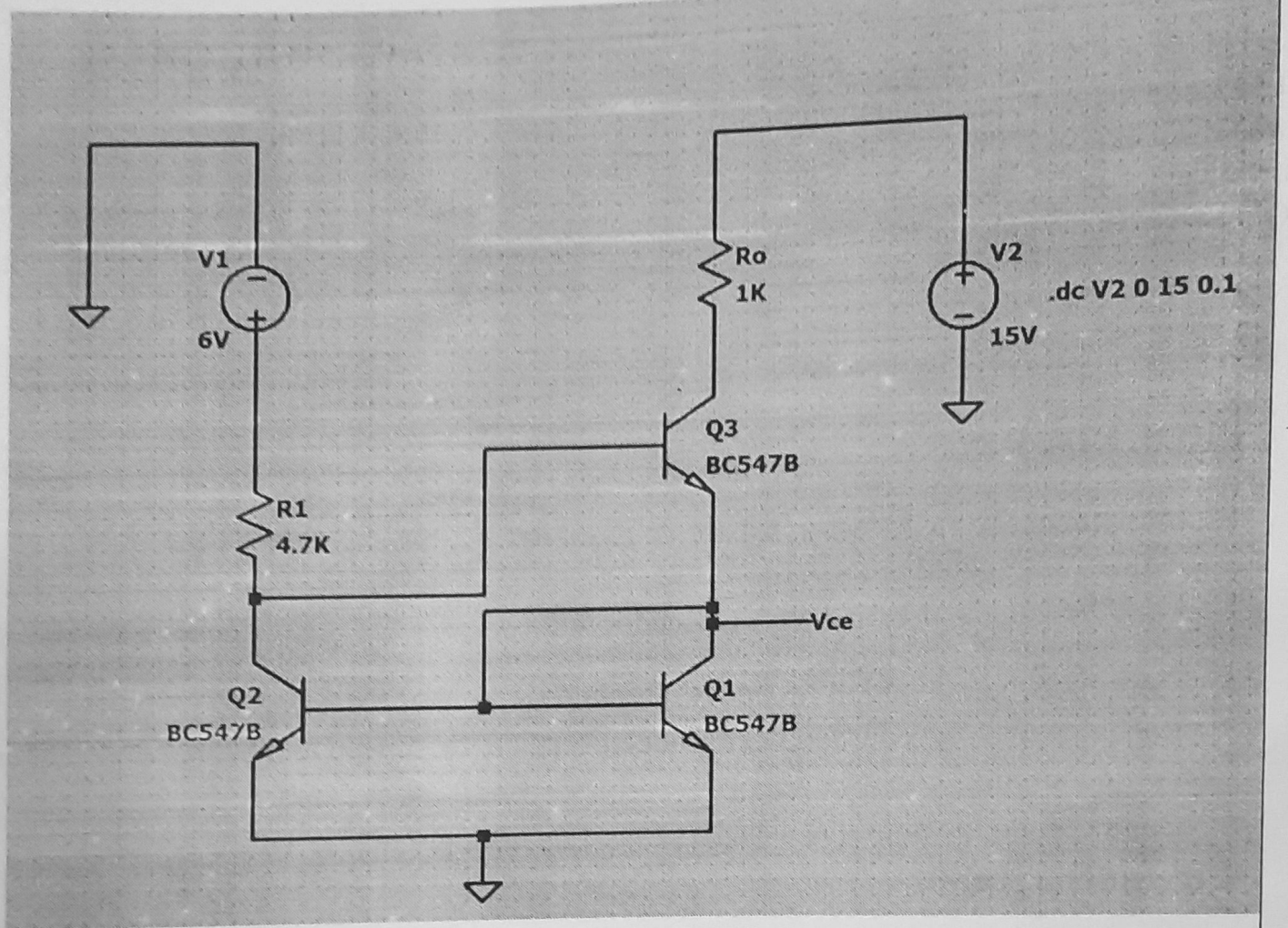


Widlar Constant Current Source

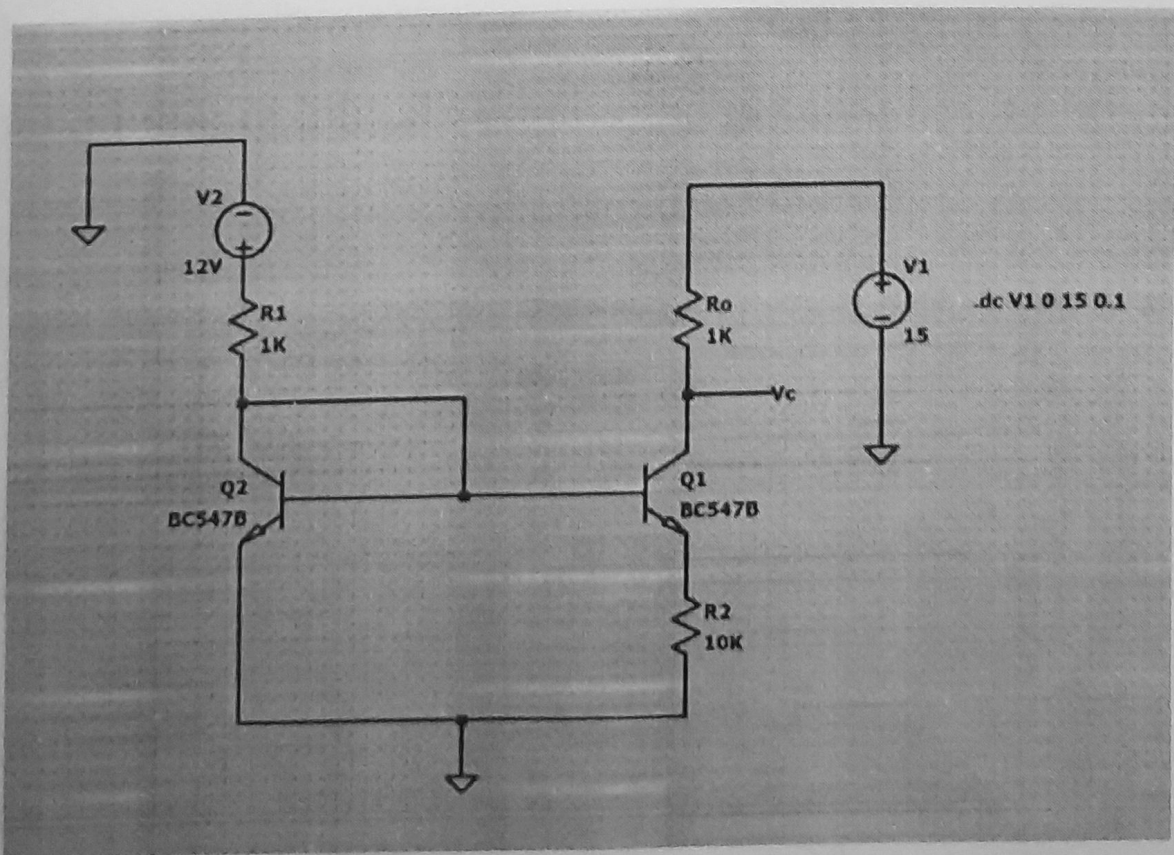


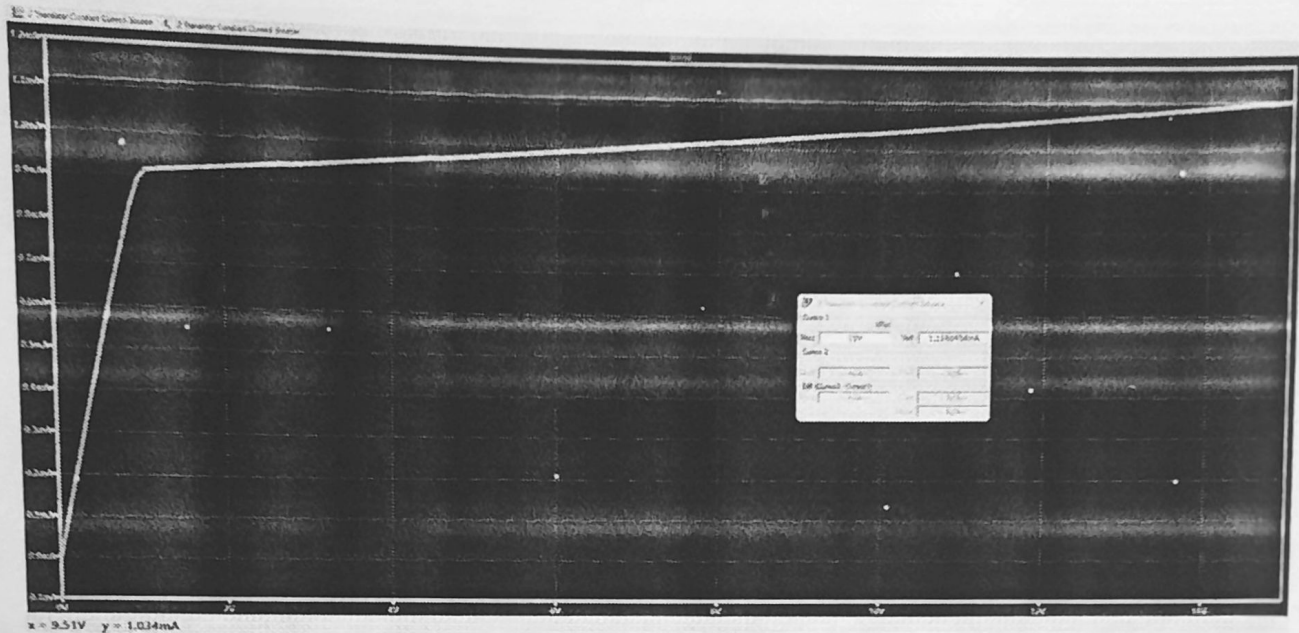Basic Two Transistor Constant Current Source



Wilson Constant Current Source

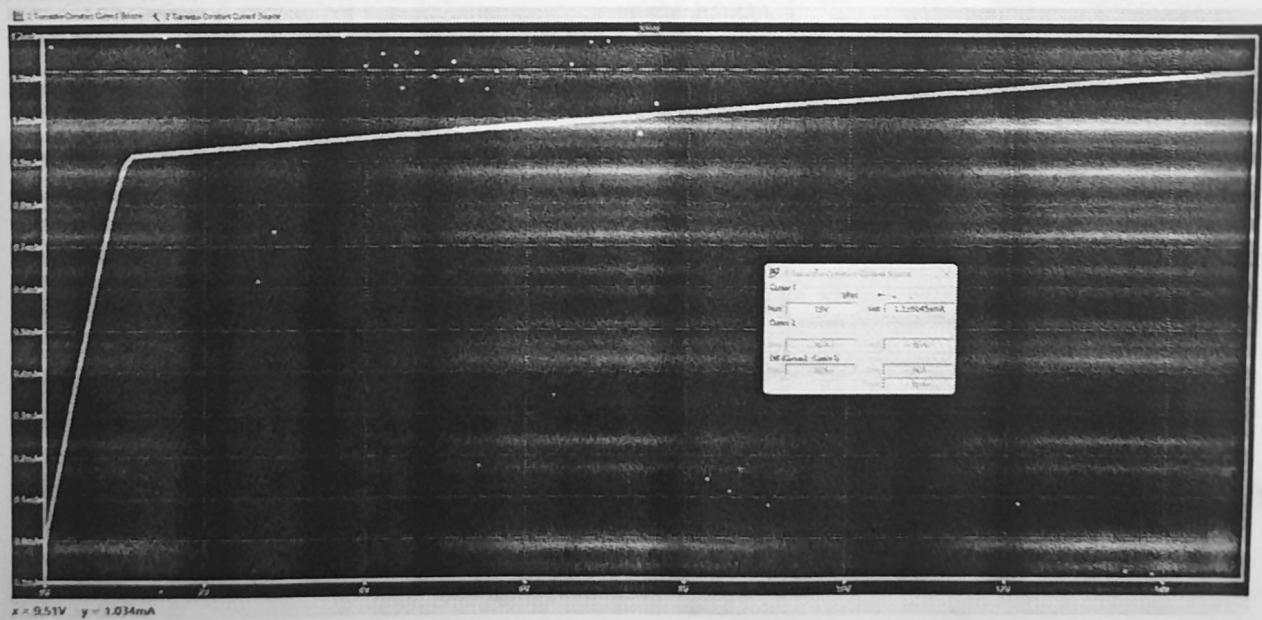

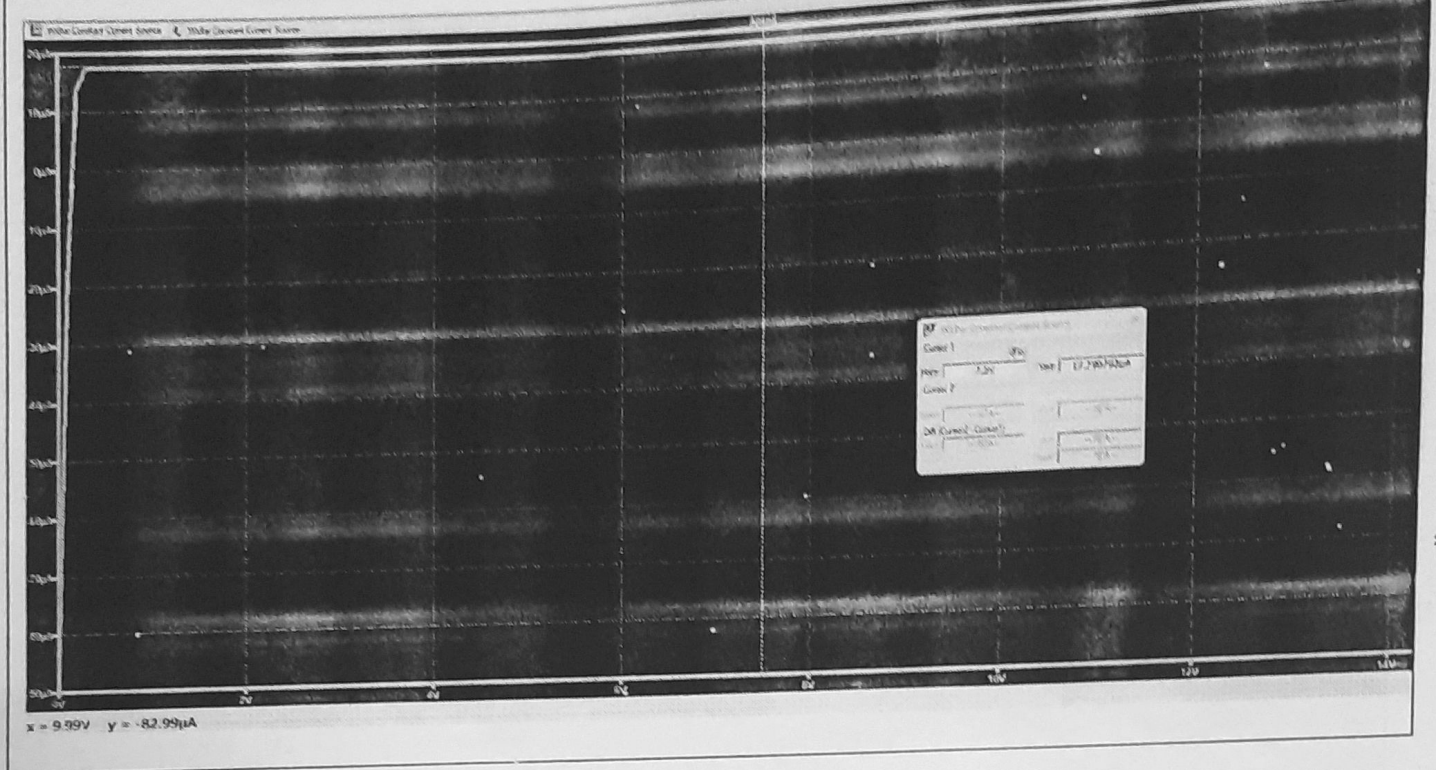

Observation Table I

Simulation		
	Output Resistance (ro)	Output Current (Io)
Basic Two transistor constant current source	69.35 KΩ	1.116 mA
Wilson constant current source	6.055 MΩ	996.95 uA
Widlar constant current source	31.456 MΩ	18.03 uA

Mathematical Analysis and Theoretical Calculations

$$\text{Slope } m = \frac{I_{O2} - I_{O1}}{V_{CC2} - V_{CC1}} \quad \left. \vphantom{\frac{I_{O2} - I_{O1}}{V_{CC2} - V_{CC1}}} \right\} \text{LT Spec}$$

$$\therefore r_o = \frac{1}{m}$$

① Basic 2-transistor constant current source:

$$r_o = \frac{1}{(1.44)(10^{-5})} = 69.35 \text{ k}\Omega$$

② Wilson Constant Current Source: $r_o = \frac{1}{(1.65)10^{-7}} = 6.055 \text{ M}\Omega$

③ Wildar Current Constant Source: $r_o = \frac{1}{(3.48)10^{-8}} = 31.456 \text{ M}\Omega$



Conclusion: Types of Constant Current Sources explained various current mirroring Techniques used to replicate current across while maintaining stability against load ~~ratio~~ variations. Using LTSpice, three specific circuits were simulated to analyze their output characteristics. The result demonstrates that ~~will~~ widlar & wilson current source provide a higher output resistance (r_o) than the basic two-transistor model, effectively counteracting Early Effect & improving performance.

Signature of faculty